



DIGITAL SYSTEM DESIGN LABORATORY

LAB 6 REPORT

SINGLE CYCLE MICROPROCESSOR DESIGN

NAME: BÙI GIA BẢO
ID: ITITIU22019

I. LAB OBJECTIVES

This Lab experiments are intended to design and test a Single Cycle Microprocessor

II. DESCRIPTION

Single Cycle Microprocessor datapath to be implemented is in figure 2.1.

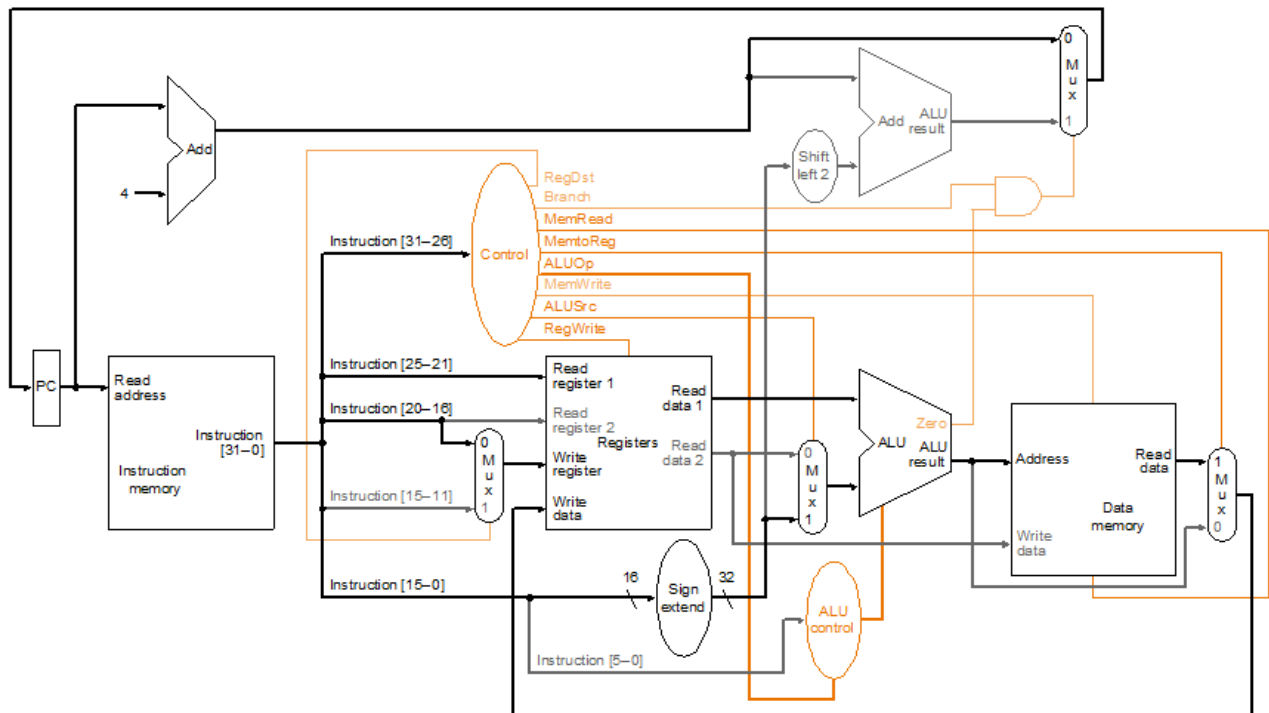


Figure 2.1: Single Cycle Microprocessor DataPath

III. LAB PROCEDURE

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To understand and write the assembly code using MIPS Instruction set

register number of MIPS compiler conventions

Name	Register number	Usage
\$zero	0	the constant value 0
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved (by callee)
\$t8-\$t9	24-25	more temporaries
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address

MIPS Assembly Language Sumarize:

MIPS assembly language				
Category	Instruction	Example	Meaning	Comments
Arithmetic	add	add \$s1, \$s2, \$s3	$\$s1 = \$s2 + \$s3$	Three operands; data in registers
	subtract	sub \$s1, \$s2, \$s3	$\$s1 = \$s2 - \$s3$	Three operands; data in registers
	add immediate	addi \$s1, \$s2, 100	$\$s1 = \$s2 + 100$	Used to add constants
Data transfer	load word	lw \$s1, 100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Word from memory to register
	store word	sw \$s1, 100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Word from register to memory
	load byte	lb \$s1, 100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Byte from memory to register
	store byte	sb \$s1, 100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Byte from register to memory
	load upper immediate	lui \$s1, 100	$\$s1 = 100 * 2^{16}$	Loads constant in upper 16 bits
Conditional branch	branch on equal	beq \$s1, \$s2, 25	if ($\$s1 == \$s2$) go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1, \$s2, 25	if ($\$s1 != \$s2$) go to PC + 4 + 100	Not equal test; PC-relative
	set on less than	slt \$s1, \$s2, \$s3	if ($\$s2 < \$s3$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than; for beq, bne
	set less than immediate	slti \$s1, \$s2, 100	if ($\$s2 < 100$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than constant
Uncondi- tional jump	jump	j 2500	go to 10000	Jump to target address
	jump register	jr \$ra	go to \$ra	For sw itch, procedure return
	jump and link	jal 2500	$\$ra = \text{PC} + 4$; go to 10000	For procedure call

Operation code (Op code) summarize:


Op	Opcode name	Value
000000	R-format	Rformat1
000010	jmp	JUMP1
000100	beq	BEQ1
100011	lw	Mem1
101011	sw	Mem1

ALU opcode and Function

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used


ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Instruction Formats

 

III.7.1 AIM: Complet Single Cycle processor 16 bit

Op	Opcode name	Value
000000	R-format	R-Type
000010	jmp	J-Type
000100	beq	I-Type
100011	lw	
101011	sw	
010000	addi	

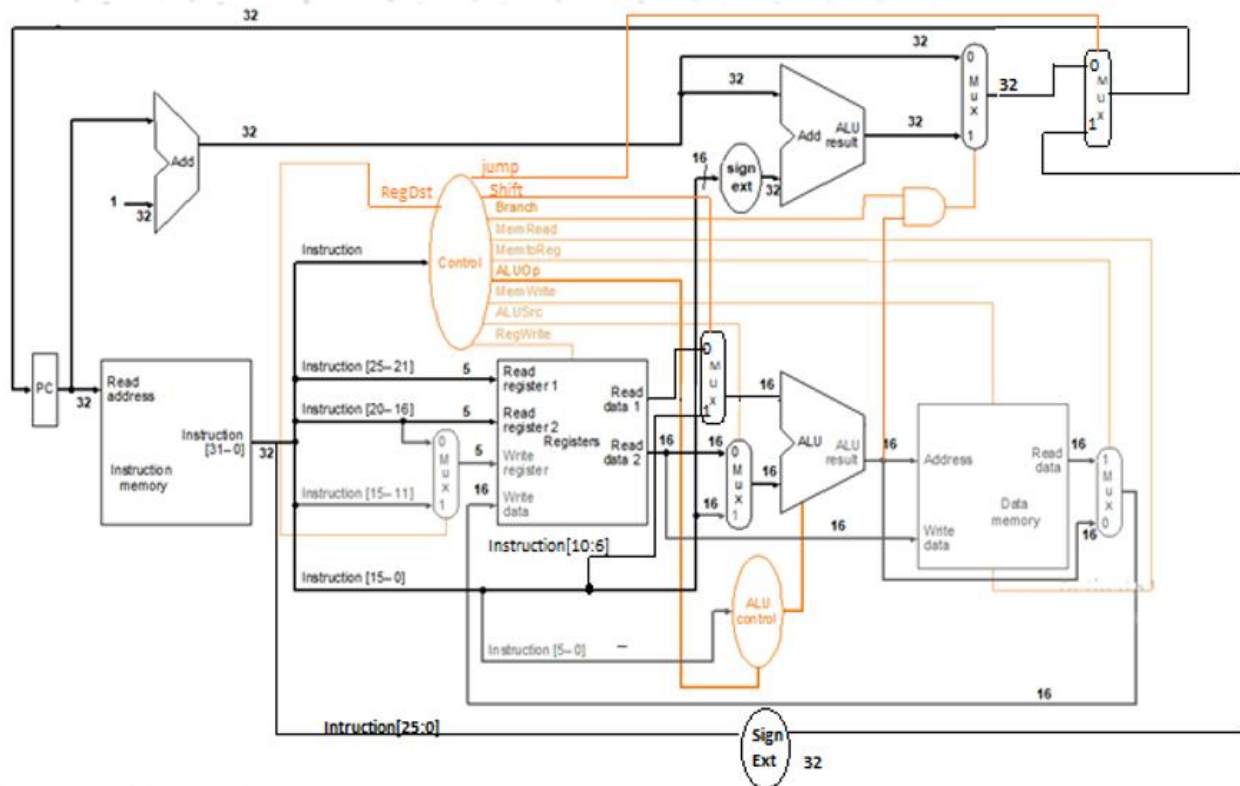

III.7.2 CODE

```

module
lab6_ex1(SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7);
    input [17:0] SW;
    output[17:0] LEDR;
    output[7:0] LEDG;

    output [0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7;
    wire[31:0] pc_out,alu_out, instr;
    reg[31:0] w_hex;

```

```
R_Type_Proc(.reset(SW[16]), .clk(SW[17]), .zero(LEDG[7]),
.Instruction(instr), .w_ALUout(alu_out), .w_pc_out(pc_out));

always @(*) begin
    case (SW[2:0])
        3'b000: w_hex = instr; // Instruction
        3'b001: w_hex = alu_out; // ALU result
        3'b010: w_hex = pc_out; // PC address
        default: w_hex = 32'b0;
    endcase
end

HEX_7SEG_DECODE H0(.BIN(w_hex[3:0]), .SSD(HEX0));
HEX_7SEG_DECODE H1(.BIN(w_hex[7:4]), .SSD(HEX1));
HEX_7SEG_DECODE H2(.BIN(w_hex[11:8]), .SSD(HEX2));
HEX_7SEG_DECODE H3(.BIN(w_hex[15:12]), .SSD(HEX3));
HEX_7SEG_DECODE H4(.BIN(w_hex[19:16]), .SSD(HEX4));
HEX_7SEG_DECODE H5(.BIN(w_hex[23:20]), .SSD(HEX5));
HEX_7SEG_DECODE H6(.BIN(w_hex[27:24]), .SSD(HEX6));
HEX_7SEG_DECODE H7(.BIN(w_hex[31:28]), .SSD(HEX7));

endmodule

module R_Type_Proc(reset, clk, zero, Instruction, w_ALUout, w_pc_out);

    input clk;
    input reset;
    output zero;

    output[31:0] Instruction;
    wire[31:0] w_pc_in;
    wire[31:0] w_mux1_out;
    output[31:0] w_pc_out;
    wire[31:0] w_pc_plus_1;
    wire[31:0] w_m2;
    wire[31:0] w_branch_add;

    wire[4:0] w_m3;
    wire[31:0] W_RD1, W_RD2;
    wire[31:0] W_MemtoReg;
```

```
wire[31:0] w_m1;
output[31:0] w_ALUout;
wire[31:0] w_RDm;

wire RegWrite;
wire ALUsrc;
wire ALUop;
wire PCsrc;
wire MemRead;
wire MemWrite;
wire MemtoReg;
wire RegDst;

Program_Counter c1(.clk(clk), .reset(reset), .PC_in(w_pc_in),
.PC_out(w_pc_out));

Adder32Bit c2(.input1(w_pc_out), .input2(32'b1), .out(w_pc_plus_1));

Mux_32_bit c3(.in0(w_pc_plus_1), .in1(w_m2), .mux_out(w_pc_in),
.select(PCsrc));

Adder32Bit c4(.input1(w_pc_plus_1), .input2(w_branch_add),
.out(w_m2));

Instruction_Memory c5(.read_address(w_pc_out), .instruction(Instruction),
.reset(reset));

Register_File c6( .clk(clk),
.read_addr_1(Instruction[25:21]),
.read_addr_2(Instruction[20:16]),
.write_addr(w_m3),
.read_data_1(W_RD1),
.read_data_2(W_RD2),
.write_data(W_MemtoReg),
.RegWrite(RegWrite));

Sign_Extension c7(.sign_in(Instruction[15:0]), .sign_out(w_branch_add));

Mux_32_bit c8(.in0(W_RD2), .in1(w_branch_add), .mux_out(w_m1),
.select(ALUsrc));
```

```

alu    c9( .alufn(ALUOp),
           .ra(W_RD1),
           .rb_or_imm(w_m1),
           .aluout(w_ALUout),
           .zero(zero));

Data_Memory c10(.addr(w_ALUout),
                .write_data(W_RD2),
                .read_data(w_RDm),
                .MemRead(MemRead),
                .MemWrite(MemWrite));

Mux_32_bit c11(.in0(w_ALUout), .in1(w_RDm),
               .mux_out(W_MemtoReg), .select(MemtoReg));

control c12(
           .op_code(Instruction[31:26]),
           .RegDst(RegDst),
           .PCsrc(PCsrc),
           .MemRead(MemRead),
           .MemtoReg(MemtoReg),
           .ALUOp(ALUOp),
           .MemWrite(MemWrite),
           .ALUsrc(ALUsrc),
           .RegWrite(RegWrite)
);

Mux_5_bit c13(.in0(Instruction[20:16]), .in1(Instruction[15:11]),
               .mux_out(w_m3), .select(RegDst));

endmodule

module HEX_7SEG_DECODE(BIN, SSD);
input [3:0] BIN;
output reg [0:6] SSD;
always begin
case(BIN)
0:SSD=7'b0000001;
1:SSD=7'b1001111;

```



```
2:SSD=7'b0010010;  
3:SSD=7'b0000110;  
4:SSD=7'b1001100;  
5:SSD=7'b0100100;  
6:SSD=7'b0100000;  
7:SSD=7'b0001111;  
8:SSD=7'b0000000;  
9:SSD=7'b0001100;  
10:SSD=7'b0001000;  
11:SSD=7'b1100000;  
12:SSD=7'b0110001;  
13:SSD=7'b1000010;  
14:SSD=7'b0110000;  
15:SSD=7'b0111000;  
endcase  
end  
endmodule  
  
module Program_Counter (clk, reset, PC_in, PC_out);  
    input clk, reset;  
    input [31:0] PC_in;  
    output reg [31:0] PC_out;  
    always @ (posedge clk or posedge reset)  
    begin  
        if(reset==1'b1)  
            PC_out<=0;  
        else  
            PC_out<=PC_in;  
        end  
    end  
endmodule  
  
module Adder32Bit(input1, input2, out);  
    input [31:0] input1, input2;  
    output [31:0] out;  
    reg [31:0]out;  
    always@(input1 or input2)  
    begin  
        out <= input1 + input2;  
    end  
endmodule
```

```

module alu(
    input [2:0] alufn,
    input [31:0] ra,
    input [31:0] rb_or_imm,
    output reg [31:0] aluout,
    output reg zero);
    parameter    ALU_OP_ADD      = 3'b000,
                  ALU_OP_SUB      = 3'b001,
                  ALU_OP_AND      = 3'b010,
                  ALU_OP_OR       = 3'b011,
                  ALU_OP_XOR      = 3'b100,
                  ALU_OP_LW       = 3'b101,
                  ALU_OP_SW       = 3'b110,
                  ALU_OP_BEQ      = 3'b111;

    always @(*)
    begin
        case(alufn)
            ALU_OP_ADD      : aluout = ra + rb_or_imm;
            ALU_OP_SUB      : aluout = ra - rb_or_imm;
            ALU_OP_AND      : aluout = ra & rb_or_imm;
            ALU_OP_OR       : aluout = ra | rb_or_imm;
            ALU_OP_XOR      : aluout = ra ^ rb_or_imm;
            ALU_OP_LW       : aluout = ra + rb_or_imm;
            ALU_OP_SW       : aluout = ra + rb_or_imm;
            ALU_OP_BEQ      : begin
                                zero = (ra==rb_or_imm)?1'b1:1'b0;
                                aluout = ra - rb_or_imm;
                            end
        endcase
    end
end
endmodule

module Register_File (clk,read_addr_1, read_addr_2, write_addr, read_data_1,
read_data_2, write_data, RegWrite);
    input [4:0] read_addr_1, read_addr_2, write_addr;
    input [31:0] write_data;
    input clk,RegWrite;
    reg checkRegWrite;
    output reg [31:0] read_data_1, read_data_2;
    reg [31:0] Regfile [31:0];
    integer k;

```

```
initial begin
for (k=0; k<32; k=k+1)
    begin
        Regfile[k] = 32'd0;
    end

end

//assign read_data_1 = Regfile[read_addr_1];
always @(read_data_1 or Regfile[read_addr_1])
    begin
        if (read_addr_1 == 0) read_data_1 = 0;
        else
            begin
                read_data_1 = Regfile[read_addr_1];
            end
    end
end
//$display("read_addr_1=%d,read_data_1=%h",read_addr_1,read_data_1);

//assign read_data_2 = Regfile[read_addr_2];
always @(read_data_2 or Regfile[read_addr_2])
    begin
        if (read_addr_2 == 0) read_data_2 = 0;
        else
            begin
                read_data_2 = Regfile[read_addr_2];
            end
    end
end
//$display("read_addr_2=%d,read_data_2=%h",read_addr_2,read_data_2);

always @(posedge clk)
    begin
        if (RegWrite == 1'b1)
            begin
                Regfile[write_addr] = write_data;
            end
    end
end
endmodule
```

```
module Data_Memory (addr, write_data, read_data, MemRead, MemWrite);
    input [31:0] addr;
    input [31:0] write_data;
    output [31:0] read_data;
    input MemRead, MemWrite;
    reg [31:0] DMemory [255:0];
    integer k;
    assign read_data = (MemRead) ? DMemory[addr] : 32'bx;
    initial begin
        for (k=0; k<64; k=k+1)
            begin
                DMemory[k] = 32'b0;
            end
        DMemory[11] = 99;
    end
    always @(*)
    begin
        if (MemWrite) DMemory[addr] = write_data;
    end
endmodule
```

```
module Sign_Extension (sign_in, sign_out);
    input [15:0] sign_in;
    output [31:0] sign_out;
    assign sign_out[15:0]=sign_in[15:0];
    assign sign_out[31:16]=sign_in[15]?16'b1111_1111_1111_1111:16'b0;
endmodule
```

```
module Mux_32_bit (in0, in1, mux_out, select);
    parameter N = 32;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select? in1: in0 ;
endmodule
```

```
module Mux_5_bit (in0, in1, mux_out, select);
    parameter N = 5;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
```

```
input select;
assign mux_out = select? in1: in0 ;
endmodule

module Instruction_Memory (read_address, instruction, reset);
input reset;
input [31:0] read_address;
output [31:0] instruction;
reg [31:0] Imemory [63:0];
integer k;
// I-MEM in this case is addressed by word, not by byte
assign instruction = Imemory[read_address];
always @(posedge reset)
begin
for (k=16; k<32; k=k+1)
begin
// here Out changes k=0 to k=16
Imemory[k] = 32'b0;
end

// addi $s2, $zero, 1
Imemory[0] = 32'b001000_00000_10010_00000000000000001;

// addi $s3, $zero, 10
Imemory[1] = 32'b001000_00000_10011_00000000000001010;

// addi $s4, $zero, 0
Imemory[2] = 32'b001000_00000_10100_00000000000000000;

// add $s4, $s2, $s4
Imemory[3] = 32'b000000_10010_10100_10100_00000_100000;

// add $s4, $s3, $s4
Imemory[4] = 32'b000000_10011_10100_10100_00000_100000;

// add $s5, $s4, $s2
Imemory[5] = 32'b000000_10100_10010_10101_00000_100000;

// rest = NOP
Imemory[6] = 32'b0;
Imemory[7] = 32'b0;
```

```
end
endmodule

module Sign_Extension_26 (sign_in, sign_out);
    input [25:0] sign_in;
    output [31:0] sign_out;
    assign sign_out[25:0]=sign_in[25:0];
    assign sign_out[31:26]=sign_in[25]?6'b111111:6'b0;
endmodule

module control(
    input [5:0] op_code,
    output reg RegDst,
    output reg PCsrc,
    output reg MemRead,
    output reg MemtoReg,
    output reg [2:0] ALUop,
    output reg MemWrite,
    output reg ALUsrc,
    output reg RegWrite
);

always @(*) begin
    // default values
    RegDst = 0;
    PCsrc = 0;
    MemRead = 0;
    MemtoReg = 0;
    ALUop = 3'b000;
    MemWrite = 0;
    ALUsrc = 0;
    RegWrite = 0;

    case(op_code)

        // R-type
        6'b000000: begin
            RegDst = 1;
            ALUop = 3'b000; // ADD
            RegWrite = 1;
        end
    end
```

```
// addi
6'b001000: begin
    ALUsrc = 1;
    ALUop = 3'b000; // ADD
    RegWrite = 1;
end

// lw
6'b100011: begin
    ALUsrc = 1;
    MemRead = 1;
    MemtoReg = 1;
    ALUop = 3'b000; // ADD
    RegWrite = 1;
end

// sw
6'b101011: begin
    ALUsrc = 1;
    MemWrite = 1;
    ALUop = 3'b000; // ADD
end

// beq
6'b000100: begin
    ALUop = 3'b001; // SUB
    PCsrc = 1;    // (should be AND with zero later)
end

// j (basic support)
6'b000010: begin
    PCsrc = 1;
end

endcase
end
endmodule
```

III.7.3 LAB ASSIGNMENT

1) Write Verilog code to implement Complete Processor module with all following instructions:

Op	Opcode name	Value
000000	R-format	R-Type
000010	jmp	J-Type
000100	beq	I-Type
100011	lw	
101011	sw	
010000	addi	

2) Write testbenches to verify Complete Processor, simulate and check the simulation output data.

3) Compile the following code into binary machine code and store in Instruction memory to test the Complete Processor.

Testing Assembly Program 1:

<u>Instruction</u>	<u>Meaning</u>
Begin:	
addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2
addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3
addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5
add \$s4, \$s2, \$s3 //	\$s4 = \$s2 + \$s3 => R20=0x77
sub \$s1, \$s2, \$s3 //	\$s1 = \$s2 - \$s3 => R17=0x22
sw \$s1, 0x02(\$s2) //	Memory[\$s2+0x02] = \$s1
lw \$s6, 0x02(\$s2) //	\$s6 = Memory[\$s2+0x02]
bne \$s5, \$s4, End //	Next instr. is at End if \$s5 != \$s4
addi \$s8, \$zero, 0x10 //	load immediate value 10 to register \$s8
beq \$s5,\$s4, End //	Next instr. is at End if \$s7 == \$s4
addi \$s8, \$zero, 0x20 //	load immediate value 20 to register \$s8
End: j End //	jump End

3) Compile the following code into binary machine code and store in Instruction memory to test the Complete Processor.

Testing Assembly Program 2:

<u>Instruction</u>	<u>Meaning</u>
Begin:	
addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2
addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3
addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5
add \$s4, \$s2, \$s3 //	\$s4 = \$s2 + \$s3 => R20=0x77
sub \$s1, \$s2, \$s3 //	\$s1 = \$s2 - \$s3 => R17=0x22
sw \$s1, 0x02(\$s2) //	Memory[\$s2+0x02] = \$s1
lw \$s6, 0x02(\$s2) //	\$s6 = Memory[\$s2+0x02]
beq \$s5,\$s4, End //	Next instr. is at End if \$s7 == \$s4



```
addi $s8, $zero, 0x10 // load immediate value 10 to register $s8
bne $s5, $s4, End // Next instr. is at End if $s5 != $s4
addi $s8, $zero, 0x20 // load immediate value 20 to register $s8
End: j End // jump End
```

III. LAB REPORT GUIDELINES

Students write up a report on the Verilog HDL implementation experiment projects created in this lab. The lab report should include Verilog code for the module under test, Verilog test bench code and a truth table results, and example data input and output to validate the experiment. Simulation Result in form of Simulation Capture Screen. The implementation results in FPGA Kit, compare the simulation results and implementation results.