



DIGITAL SYSTEM DESIGN LABORATORY

REPORT LAB 2

IMPLEMENTATION OF SEQUENTIAL LOGIC CIRCUITS USING VERILOG AND VHDL IN FPGA KIT

NAME: Bùi Gia Bảo

ID: ITITIU22019

I. LAB OBJECTIVES


This Lab experiments are intended to implement Basic Sequential Circuits in Verilog. Students are required to write test bench to simulate the given example code and Top level module to implement these codes in DE2-115 FPGA Kit.

II. LAB EXPERIMENT EXERCISES

AIM: WRITE VHDL OR VHDL CODES TO SIMULATE AND IMPLEMENT THE FOLLOWING DIGITAL SEQUENTIAL LOGIC CIRCUITS:

 - 1) DFF with Asynchronous Reset using Verilog
- 2) DFF with Synchronous Reset using VHDL
- 3) JK Flip Flop VHDL
- 4) Asynchronous Counter 4-bit using VHDL structural modeling
- 5) Asynchronous Counter 8-bit using VHDL behavior modeling
- 6) Synchronous Counter 4-bit using Verilog structural modeling
- 7) Synchronous Counter n-bit VHDL behavior modeling
- 8) Right Shift Register 4-bit using Verilog structural modeling
- 9) Left Shift Register 4-bit VHDL structural modeling
- 10) Universal Shift Register N-bit Verilog behavior modeling
- 11) Universal Shift Register N-bit VHDL behavior modeling

1/ DFF with Asynchronous Reset using Verilog



Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

CODE

```
module lab2_ex1(SW,LEDG,LEDR);
    input[2:0] SW;
    output [1:0] LEDG;
    output [2:0] LEDR;
    assign LEDR=SW;

    dff_async_reset test(SW[0],SW[1],SW[2],LEDG[0]);
endmodule


module dff_async_reset (
    input wire data,    // Data input

    input wire reset,   // Asynchronous reset input
    input wire clk,     // Clock input
    output reg q        // Output
);

    always @ (posedge clk or negedge reset) begin
        // If reset is active (assuming active-low reset)
        if (~reset) begin
            q <= 1'b0;    // Reset the output
        end else begin
            q <= data;    // Capture the data on the clock edge
        end
    end
end
```

endmodule

2/ DFF with Synchronous Reset using VHDL

 

CLK	RST	D	Q (Next State)	Q' (Next State)	Description
↑	0	0	0	1	Normal operation: Data '0' loads into Q.
↑	0	1	1	0	Normal operation: Data '1' loads into Q.
↑	1	X	0	1	Synchronous Reset: Q is forced to '0', ignoring D.
↓	X	X	Q (Current)	Q' (Current)	No change on falling edge (X = Don't Care).
X	X	X	Q (Current)	Q' (Current)	No change between clock edges (X = Don't Care).

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity ex2_vhdl is
```

```
Port (
```

```
    SW : in STD_LOGIC_VECTOR(2 downto 0); -- SW(0)=clk, SW(1)=reset, SW(2)=D
```



```
    LEDG : out STD_LOGIC_VECTOR(1 downto 0);  
    LEDR : out STD_LOGIC_VECTOR(2 downto 0)  
);  
end ex2_vhdl;
```

architecture Structural of ex2_vhdl is


```
-- Internal component declaration for DFF  
component dff_sync  
  Port (  
    clk : in STD_LOGIC;  
    reset : in STD_LOGIC;  
    d : in STD_LOGIC;  
    q : out STD_LOGIC  
  );  
end component;  
  
begin  
  -- Connect switches to red LEDs  
  LEDR <= SW;  
  
  -- Instantiate D Flip-Flop (Synchronous Reset)  
  test: dff_sync  
    port map (  
      clk => SW(0),  
      reset => SW(1),  
      d => SW(2),  
      q => LEDG(0)  
    );  
  
  -- Unused green LED output (set to 0)  
  LEDG(1) <= '0';  
  
end Structural;
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity dff_sync is  
  Port (  
    clk : in STD_LOGIC;  
    reset : in STD_LOGIC;  
    d : in STD_LOGIC;  
    q : out STD_LOGIC  
  );  
end dff_sync;
```

```
architecture Behavioral of dff_sync is
  signal q_reg : STD_LOGIC := '0';
begin
  process (clk)
  begin
    if rising_edge(clk) then
      if reset = '1' then
        q_reg <= '0';
      else
        q_reg <= d;
      end if;
    end if;
  end process;
  q <= q_reg;
end Behavioral;
```

3/ JK Flip Flop VHDL

 

INPUT		OUTPUT	
Q _n	Q _(n+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- =====
-- Top-Level Entity: ex3_vhdl
-- Description: JK Flip-Flop with Asynchronous Reset
-- =====

entity ex3_vhdl is
  Port (
    SW : in STD_LOGIC_VECTOR(3 downto 0); -- SW(0)=CLK, SW(1)=J, SW(2)=K,
    SW(3)=RESET
    LEDG : out STD_LOGIC_VECTOR(1 downto 0); -- LEDG(0)=Q, LEDG(1)=Q'
    LEDR : out STD_LOGIC_VECTOR(3 downto 0) -- Mirrors SW
  );
end ex3_vhdl;

architecture Structural of ex3_vhdl is
  -- Component declaration for JK Flip-Flop
  component jk_ff
    Port (
      clk : in STD_LOGIC;
      j : in STD_LOGIC;
      k : in STD_LOGIC;
      reset : in STD_LOGIC; -- Active-high asynchronous reset
      q : out STD_LOGIC
    );
  end component;

  signal Q_sig : STD_LOGIC;

```

```
begin
  -- Connect switches to red LEDs
  LEDR <= SW;

  -- Instantiate JK Flip-Flop
  DUT: jk_ff
    port map (
      clk  => SW(0),
      j    => SW(1),
      k    => SW(2),
      reset => SW(3),
      q    => Q_sig
    );

  -- Output Q and its complement
  LEDG(0) <= Q_sig;
  LEDG(1) <= not Q_sig;

end Structural;

-- =====
-- Submodule: JK Flip-Flop (Asynchronous Reset)
-- =====

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity jk_ff is
  Port (
    clk  : in  STD_LOGIC;
    j    : in  STD_LOGIC;
    k    : in  STD_LOGIC;
    reset : in  STD_LOGIC;
    q     : out STD_LOGIC
  );
end jk_ff;

architecture Behavioral of jk_ff is
  signal q_reg : STD_LOGIC := '0';
  signal jk_vec : STD_LOGIC_VECTOR(1 downto 0);
begin
  jk_vec <= j & k; -- Explicitly make a 2-bit vector

  process (clk, reset)
  begin
    if reset = '1' then
      q_reg <= '0';          -- Asynchronous reset
```



```


elsif rising_edge(clk) then
  case jk_vec is
    when "00" => q_reg <= q_reg; -- No change
    when "01" => q_reg <= '0'; -- Reset
    when "10" => q_reg <= '1'; -- Set
    when "11" => q_reg <= not q_reg; -- Toggle
    when others => null;
  end case;
end if;
end process;

q <= q_reg;
end Behavioral;

```

4/ Asynchronous Counter 4-bit using VHDL structural modeling

A four-bit “up” counter

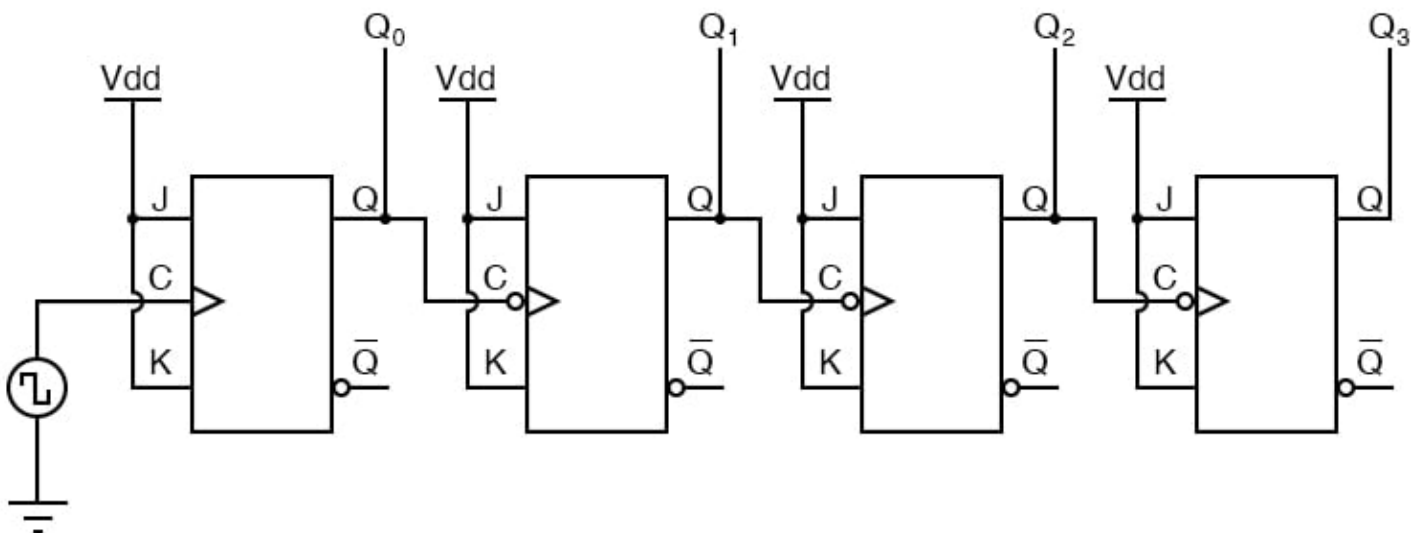

CK	Q ₃	Q ₂	Q ₁	Q ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	1	1	1	1
1	0	0	0	1	1	1	1	0
2	0	0	1	0	1	1	0	1
3	0	0	1	1	1	1	0	0
4	0	1	0	0	1	0	1	1
5	0	1	0	1	1	0	1	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	0	1	1	1
9	1	0	0	1	0	1	1	0
10	1	0	1	0	0	1	0	1
11	1	0	1	1	0	1	0	0
12	1	1	0	0	0	0	1	1
13	1	1	0	1	0	0	1	0
14	1	1	1	0	0	0	0	1
15	1	1	1	1	0	0	0	0

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ex4_vhdl is
  port (
    CLOCK_50 : in STD_LOGIC;      -- 50 MHz clock input
    SW       : in STD_LOGIC_VECTOR(0 downto 0); -- SW(0) = active-low reset
    LEDG     : out STD_LOGIC_VECTOR(3 downto 0); -- 4-bit counter output
    LEDR     : out STD_LOGIC_VECTOR(0 downto 0) -- mirror reset switch
  );
end ex4_vhdl;

architecture rtl of ex4_vhdl is

  signal clk_1Hz : STD_LOGIC := '0';
  signal q       : STD_LOGIC_VECTOR(3 downto 0) := (others => '0');

begin

  -- Mirror reset switch on LEDR
  LEDR <= SW;

  -- Instantiate 1 Hz Clock Divider
  Divider: entity work.clock_divider_1Hz

```

```
port map (  
    clk_in => CLOCK_50,  
    reset_n => SW(0),  
    clk_out => clk_1Hz  
);  
  
-- Asynchronous Ripple Counter  
process(clk_1Hz, SW)  
begin  
    if SW(0) = '0' then  
        q(0) <= '0';  
    elsif rising_edge(clk_1Hz) then  
        q(0) <= not q(0);  
    end if;  
end process;  
  
process(q(0), SW)  
begin  
    if SW(0) = '0' then  
        q(1) <= '0';  
    elsif falling_edge(q(0)) then  
        q(1) <= not q(1);  
    end if;  
end process;  
  
process(q(1), SW)  
begin  
    if SW(0) = '0' then  
        q(2) <= '0';  
    elsif falling_edge(q(1)) then  
        q(2) <= not q(2);  
    end if;  
end process;  
  
process(q(2), SW)  
begin  
    if SW(0) = '0' then  
        q(3) <= '0';  
    elsif falling_edge(q(2)) then  
        q(3) <= not q(3);  
    end if;  
end process;  
  
LEDG <= q;  
  
end rtl;
```

```
--=====
-- 50 MHz to 1 Hz Clock Divider
--=====
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity clock_divider_1Hz is
    port (
        clk_in : in STD_LOGIC;
        reset_n : in STD_LOGIC; -- Active-low reset
        clk_out : out STD_LOGIC
    );
end clock_divider_1Hz;


architecture rtl of clock_divider_1Hz is
    signal count : unsigned(25 downto 0) := (others => '0');
    signal clk_reg : STD_LOGIC := '0';
begin

    process(clk_in, reset_n)
    begin
        if reset_n = '0' then
            count <= (others => '0');
            clk_reg <= '0';
        elsif rising_edge(clk_in) then
            if count = 24999999 then -- Toggle every 0.5s for 1Hz period
                count <= (others => '0');
                clk_reg <= not clk_reg;
            else
                count <= count + 1;
            end if;
        end if;
    end process;

    clk_out <= clk_reg;

end rtl;
```

 5/ Asynchronous Counter 8-bit using VHDL behavior modeling



CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ex5_vhdl is
    port (
        CLOCK_50 : in  STD_LOGIC;      -- 50 MHz clock input
        SW       : in  STD_LOGIC_VECTOR(0 downto 0); -- SW(0) = active-low reset
        LEDG     : out STD_LOGIC_VECTOR(7 downto 0); -- 4-bit counter output
        LEDR     : out STD_LOGIC_VECTOR(0 downto 0) -- mirror reset switch
    );
end ex5_vhdl;

architecture rtl of ex5_vhdl is

    signal clk_1Hz : STD_LOGIC := '0';
    signal q       : STD_LOGIC_VECTOR(7 downto 0) := (others => '0');

begin

    -- Mirror reset switch on LEDR
    LEDR <= SW;

    -- Instantiate 1 Hz Clock Divider
    Divider: entity work.clock_divider_1Hz
        port map (
            clk_in  => CLOCK_50,
            reset_n => SW(0),
            clk_out => clk_1Hz
        );

    -- Asynchronous Ripple Counter
    process(clk_1Hz, SW)
    begin
        if SW(0) = '1' then
            q(0) <= '0';
        end if
    end process
end rtl;
```

```
    elsif rising_edge(clk_1Hz) then  
        q(0) <= not q(0);  
    end if;  
end process;
```

```
process(q(0), SW)  
begin  
    if SW(0) = '1' then  
        q(1) <= '0';  
    elsif falling_edge(q(0)) then  
        q(1) <= not q(1);  
    end if;  
end process;
```

```
process(q(1), SW)  
begin  
    if SW(0) = '1' then  
        q(2) <= '0';  
    elsif falling_edge(q(1)) then  
        q(2) <= not q(2);  
    end if;  
end process;
```

```
process(q(2), SW)  
begin  
    if SW(0) = '1' then  
        q(3) <= '0';  
    elsif falling_edge(q(2)) then  
        q(3) <= not q(3);  
    end if;  
end process;
```

```
process(q(3), SW)  
begin  
    if SW(0) = '1' then  
        q(4) <= '0';  
    elsif falling_edge(q(3)) then  
        q(4) <= not q(4);  
    end if;  
end process;
```

```
process(q(4), SW)  
begin  
    if SW(0) = '1' then  
        q(5) <= '0';  
    elsif falling_edge(q(4)) then  
        q(5) <= not q(5);  
    end if;
```

end process;

```
process(q(5), SW)
begin
    if SW(0) = '1' then
        q(6) <= '0';
    elsif falling_edge(q(5)) then
        q(6) <= not q(6);
    end if;
end process;
```

```
process(q(6), SW)
begin
    if SW(0) = '1' then
        q(7) <= '0';
    elsif falling_edge(q(6)) then
        q(7) <= not q(7);
    end if;
end process;
```

LEDG <= q;

end rtl;

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
```

```
entity clock_divider_1Hz is
    port (
        clk_in : in STD_LOGIC;
        reset_n : in STD_LOGIC; -- Active-low reset
        clk_out : out STD_LOGIC
    );
end clock_divider_1Hz;
```

```
architecture rtl of clock_divider_1Hz is
    signal count : unsigned(25 downto 0) := (others => '0');
    signal clk_reg : STD_LOGIC := '0';
begin
```

```
    process(clk_in, reset_n)
    begin
        if reset_n = '1' then
            count <= (others => '0');
            clk_reg <= '0';
```

```


    elsif rising_edge(clk_in) then
        if count = 24999999 then -- Toggle every 0.5s for 1Hz period
            count <= (others => '0');
            clk_reg <= not clk_reg;
        else
            count <= count + 1;
        end if;
    end if;
end process;

clk_out <= clk_reg;

end rtl;


```

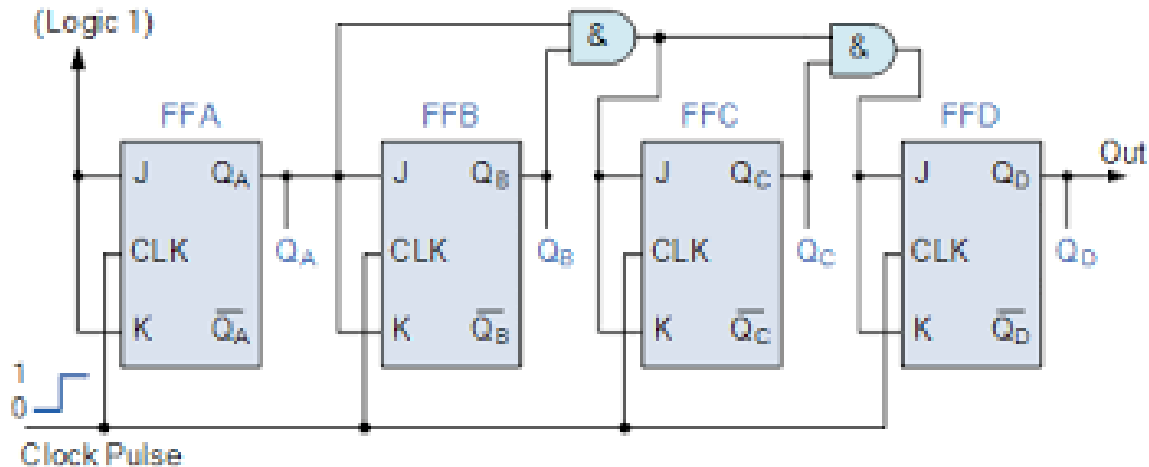6/ Synchronous Counter 4-bit using Verilog structural modeling



7/ Synchronous Counter n-bit VHDL behavior modeling

 8/ Right Shift Register 4-bit using Verilog structural modeling



```
module ex8_verilog(SW, LEDG, LEDR);
```



```
input [3:0] SW;    // SW[0]=CLK, SW[1]=d, SW[2]=input, SW[3]=ASYNC_RESET
output [3:0] LEDG; // LEDG[0]=Q, LEDG[1]=Q'
output [3:0] LEDR; // Mirrors switch input
```

```
assign LEDR = SW;
wire q0, q1, q2, q3;
wire d0, d1, d2, d3;
```

```
assign d3 = SW[2];
assign d2 = q3;
assign d1 = q2;
assign d0 = q1;
```

```
// Instantiate JK Flip-Flop
```

```
jkff_structural JK3 (
```

```
    .clk(SW[0]),
    .d(d3),
    .reset(SW[3]),
    .q(q3),
    .qbar(Qbar)
```

```
);
```

```
jkff_structural JK2 (
```

```
    .clk(SW[0]),
    .d(d2),
    .reset(SW[3]),
    .q(q2),
    .qbar(Qbar)
```

```
);
```

```
jkff_structural JK1 (
```

```
    .clk(SW[0]),
    .d(d1),
    .reset(SW[3]),
    .q(q1),
    .qbar(Qbar)
```

```
);
```

```
jkff_structural JK0 (
```

```
    .clk(SW[0]),
    .d(d0),
    .reset(SW[3]),
    .q(q0),
    .qbar(Qbar)
```

```
);
```

```
assign LEDG = {q3,q2,q1,q0};
```

```
endmodule
```

```

module jkff_structural(
    input clk, d, reset,
    output q, qbar
);
    wire jn, kn, dnot;
    wire s1, r1, s2, r2;
    wire qm, qmb; // master latch output

    // Invert reset
    wire nreset;
    not (nreset, reset);
    not(dnot,d);


    // Input gating for master latch
    nand (s1, d, qmb, clk);
    nand (r1, dnot, qm, clk);

    // Master latch
    nand (qm, s1, qmb, nreset);
    nand (qmb, r1, qm, nreset);

    // Slave latch (triggered on inverted clock)
    nand (s2, qm, ~clk);
    nand (r2, qmb, ~clk);
    nand (q, s2, qbar, nreset);
    nand (qbar, r2, q, nreset);
endmodule

```

 9/ Left Shift Register 4-bit VHDL structural modeling



CODE

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

--=====
-- D-type JK-style flip-flop (structural form, no qbar)
--=====

```

entity jkff_structural is

```
port (  
    clk : in std_logic;  
    d   : in std_logic;  
    reset : in std_logic;  
    q    : out std_logic  
);
```

end jkff_structural;

architecture structural of jkff_structural is

```
    signal nreset, dnot : std_logic;  
    signal s1, r1, s2, r2 : std_logic;  
    signal qm, qmb : std_logic;
```

begin

```
    nreset <= not reset;  
    dnot  <= not d;
```

```
-- Input gating for master latch
```

```
s1 <= not (d and qmb and clk);  
r1 <= not (dnot and qm and clk);
```

```
-- Master latch
```

```
qm <= not (s1 and qmb and nreset);  
qmb <= not (r1 and qm and nreset);
```

```
-- Slave latch (triggered on inverted clock)
```

```
s2 <= not (qm and (not clk));  
r2 <= not (qmb and (not clk));  
q  <= not (s2 and r2 and nreset);
```

end structural;

```
--=====
```

```
-- Top-level module (equivalent to ex9_verilog)
```

```
--=====
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity ex9_vhdl is

```
port (  
    SW : in std_logic_vector(3 downto 0); -- SW[0]=CLK, SW[1]=d, SW[2]=input,  
    SW[3]=ASYNC_RESET  
    LEDG : out std_logic_vector(3 downto 0); -- Q outputs  
    LEDR : out std_logic_vector(3 downto 0) -- Mirrors switch input  
);  
end ex9_vhdl;
```

architecture behavioral of ex9_vhdl is

```
signal q0, q1, q2, q3 : std_logic;
signal d0, d1, d2, d3 : std_logic;
begin
    LEDR <= SW;

    d3 <= SW(2);
    d2 <= q3;
    d1 <= q2;
    d0 <= q1;

    -- Instantiate Flip-Flops
    JK3: entity work.jkff_structural
        port map(clk => SW(0), d => d3, reset => SW(3), q => q3);

    JK2: entity work.jkff_structural
        port map(clk => SW(0), d => d2, reset => SW(3), q => q2);

    JK1: entity work.jkff_structural
        port map(clk => SW(0), d => d1, reset => SW(3), q => q1);

    JK0: entity work.jkff_structural
        port map(clk => SW(0), d => d0, reset => SW(3), q => q0);

    -- Output assignment
    LEDG <= (q3 & q2 & q1 & q0);
end behavioral;
```

10/ Universal Shift Register N-bit Verilog behavior modeling

11/ Universal Shift Register N-bit VHDL behavior modeling

