



DIGITAL SYSTEM DESIGN LABORATORY

REPORT LAB 4

BASIC BUILDING BLOCKS OF SINGLE CYCLE MICROPROCESSOR

Name: Bùi Gia Bảo
ID: ITITIU22019

I. LAB OBJECTIVES

This Lab experiments are intended to implement basic building blocks of Single Cycle Microprocessor

II. DESCRIPTION

Single Cycle Microprocessor datapath to be implemented is in figure 2.1.


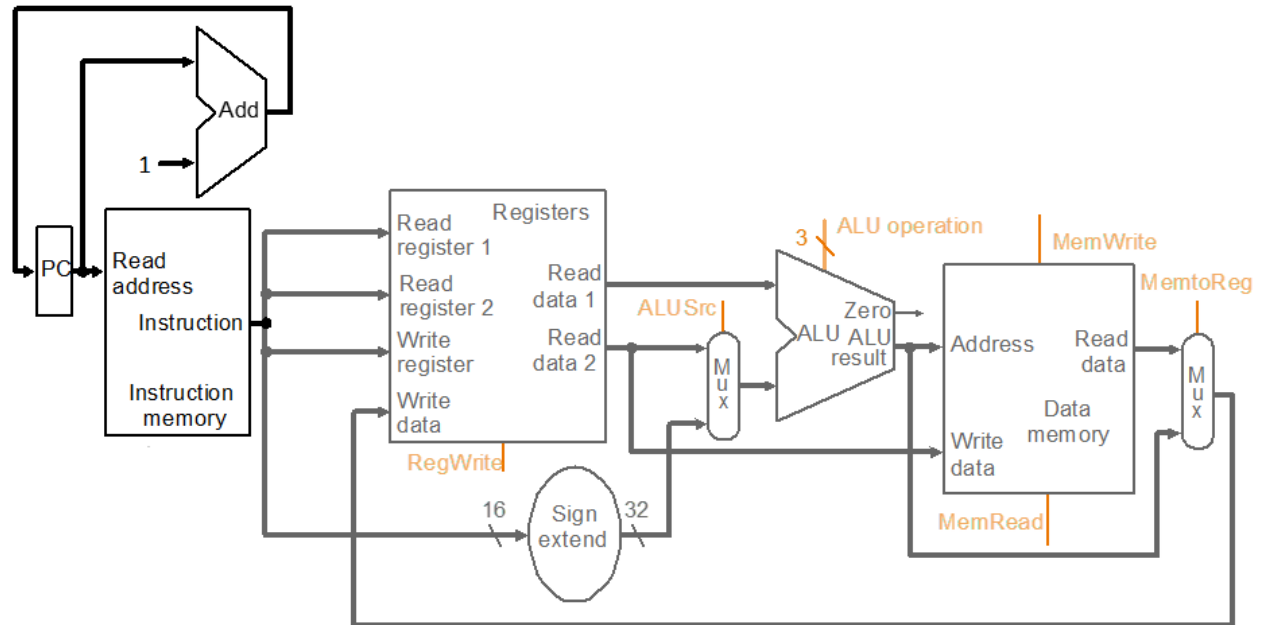


Figure 2.1: Single Cycle Microprocessor DataPath

III. LAB PROCEDURE

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To implement Program Counter

 

III.1.2 CODE

```
module Program_Counter (clk, reset, PC_in, PC_out);  
    input clk, reset;  
    input [7:0] PC_in;  
    output [7:0] PC_out;  
    reg [7:0] PC_out;  
    always @ (posedge clk or posedge reset)  
    begin  
        if(reset==1'b1)  
            PC_out<=8'b0;  
        else  
            PC_out<=PC_in;  
        end  
    end  
endmodule
```

III.1.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT


```
module lab4_pc(SW,LEDG,LEDR);  
    input[17:0] SW;  
    output[7:0] LEDG;
```

```
output[17:0] LEDR;
assign LEDR=SW;
Program_Counter (.clk(SW[0]), .reset(SW[1]), .PC_in(SW[9:2]),
.PC_out(LEDG[7:0]));
endmodule
```

```
module Program_Counter (clk, reset, PC_in, PC_out);
input clk, reset;
input [7:0] PC_in;
output [7:0] PC_out;
reg [7:0] PC_out;
always @ (posedge clk or posedge reset)
begin
    if(reset==1'b1)
        PC_out<=8'b0;
    else
        PC_out<=PC_in;
    end
end
endmodule
```

III.2 EXPERIMENT NO. 2

III.2.1 AIM: To implement 32 bit Adder

 

III.2.2 CODE

```
module Adder32Bit(input1, input2, out);  
  
    input [7:0] input1, input2;  
    output [7:0] out;  
    reg [7:0]out;  
    always@( input1 or input2)  
    begin  
        out <= input1 + input2;  
    end  
endmodule
```

III.2.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

```
module lab4_adder(SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5);  
    input[17:0] SW;  
    output[7:0] LEDG;  
    output[17:0] LEDR;  
  
    output[0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5;  
    wire [7:0] A,B,SUM;  
    assign B = SW[15:8];  
    assign A = SW[7:0];  
    Adder_8_Bit DUT(.input1(A), .input2(B), .out(SUM));  
  
    HEX_7SEG_DECODE H0(.BIN(A[3:0]), .SSD(HEX0));  
    HEX_7SEG_DECODE H1(.BIN(A[7:4]), .SSD(HEX1));  
    HEX_7SEG_DECODE H2(.BIN(B[3:0]), .SSD(HEX2));  
    HEX_7SEG_DECODE H3(.BIN(B[7:4]), .SSD(HEX3));  
    HEX_7SEG_DECODE H4(.BIN(SUM[3:0]), .SSD(HEX4));  
    HEX_7SEG_DECODE H5(.BIN(SUM[7:4]), .SSD(HEX5));  
  
endmodule
```

```
module Adder_8_Bit(input1, input2, out);  
  
    input [7:0] input1, input2;  
    output [7:0] out;  
  
    assign    out = input1 + input2;
```


```
endmodule

module HEX_7SEG_DECODE(BIN, SSD);
  input [15:0] BIN;
  output reg [0:6] SSD;

  always begin
    case(BIN)
      0:SSD=7'b0000001;
      1:SSD=7'b1001111;
      2:SSD=7'b0010010;
      3:SSD=7'b0000110;
      4:SSD=7'b1001100;
      5:SSD=7'b0100100;
      6:SSD=7'b0100000;
      7:SSD=7'b0001111;
      8:SSD=7'b0000000;
      9:SSD=7'b0001100;
      10:SSD=7'b0001000;
      11:SSD=7'b1100000;
      12:SSD=7'b0110001;
      13:SSD=7'b1000010;
      14:SSD=7'b0110000;
      15:SSD=7'b0111000;
    endcase
  end
endmodule
```

III.3 EXPERIMENT NO. 3

III.3.1 AIM: To implement the datapath for $PC = PC + 1$

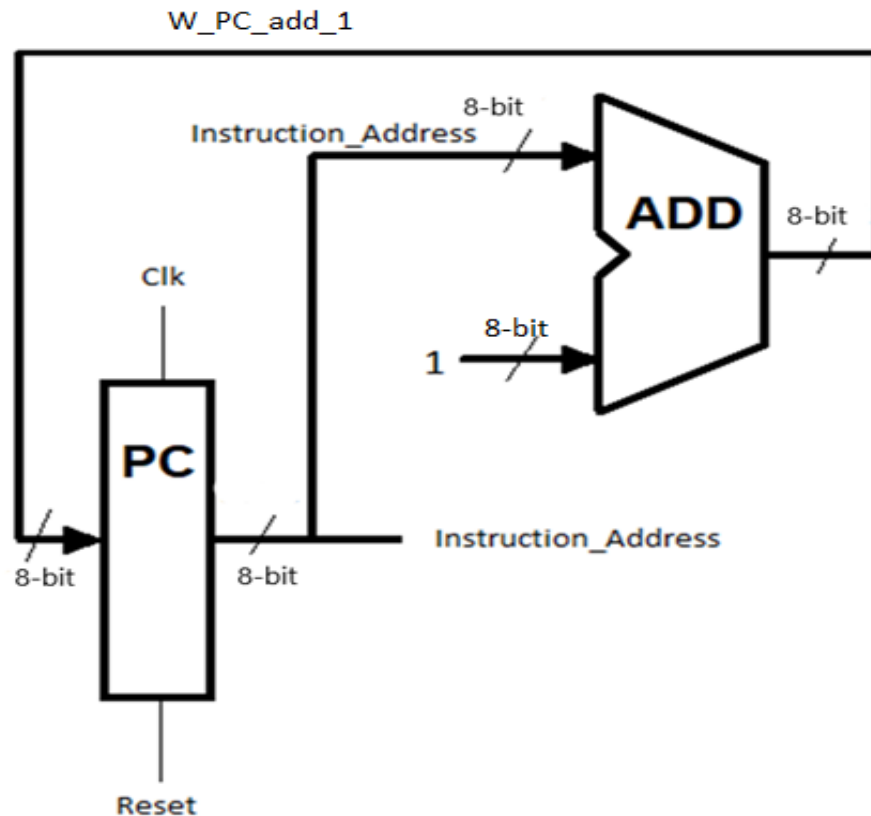

III.3.2 CODE

```

module
lab4_ex3(CLOCK_50,SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5);
    input [17:0] SW;
    input CLOCK_50;
    output[17:0] LEDR;
    output[7:0] LEDG;
    output[6:0] HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;
    wire clk_1Hz;
    clock_divider_1Hz div1 (
        .clk_in(CLOCK_50),
        .reset(SW[1]), // SW[2] = reset
        .clk_out(clk_1Hz)
    );
    PC_add_1 DUT (.clk(clk_1Hz), .reset(SW[1]),
        .Instruction_Address(LEDG[7:0]));

    hex7seg h4(LEDG[3:0], HEX4);
    hex7seg h5(LEDG[7:4], HEX5);

endmodule
    
```

```
module PC_add_1 (clk, reset, Instruction_Address);
    input clk, reset;
    output [7:0] Instruction_Address;

    wire [7:0] add_out;

    PC pc1(.clk(clk), .reset(reset), .PC_in(add_out),
    .PC_out(Instruction_Address));
    ADD add1(.input1(Instruction_Address), .input2(8'b0000_0001),
    .out(add_out));
endmodule
```

```
module hex7seg(
    input wire [3:0] hex,
    output reg [6:0] seg
);
    always @(*) begin
        case (hex)
            4'h0: seg = 7'b1000000;
            4'h1: seg = 7'b1111001;
            4'h2: seg = 7'b0100100;
            4'h3: seg = 7'b0110000;
            4'h4: seg = 7'b0011001;
            4'h5: seg = 7'b0010010;
            4'h6: seg = 7'b0000010;
            4'h7: seg = 7'b1111000;
            4'h8: seg = 7'b0000000;
            4'h9: seg = 7'b0010000;
            4'hA: seg = 7'b0001000;
            4'hB: seg = 7'b0000011;
            4'hC: seg = 7'b1000110;
            4'hD: seg = 7'b0100001;
            4'hE: seg = 7'b0000110;
            4'hF: seg = 7'b0001110;
            default: seg = 7'b1111111;
        endcase
    end
endmodule
```

```
module ADD(input1, input2, out);
```



```
input [7:0] input1, input2;  
output [7:0] out;  
  
assign out = input1 + input2;
```

```
endmodule
```

```
module PC (clk, reset, PC_in, PC_out);  
    input clk, reset;  
    input [7:0] PC_in;  
    output [7:0] PC_out;  
    reg [7:0] PC_out;  
    always @(posedge clk or posedge reset)  
    begin  
        if(reset==1'b1)  
            PC_out<=8'b0;  
        else  
            PC_out<=PC_in;  
        end  
    end  
endmodule
```

```
module clock_divider_1Hz (  
    input clk_in,  
    input reset,  
    output reg clk_out  
);  
    reg [25:0] count;  
  
    always @(posedge clk_in or posedge reset) begin  
        if (reset) begin  
            count <= 26'd0;  
            clk_out <= 1'b0;  
        end else begin  
            if (count == 26'd24_999_999) begin  
                clk_out <= ~clk_out;  
                count <= 26'd0;  
            end else begin  
                count <= count + 1;  
            end  
        end  
    end
```


```

end
end
end
endmodule

```

III.4 EXPERIMENT NO. 4

III.4.1 AIM: To implement the Instruction memory

 

III.4.2 CODE

```

module Instruction_Memory (read_address, instruction, reset);
    input reset;
    input [9:0] read_address;
    output [15:0] instruction;
    reg [15:0] Imemory [1024:0];

    Imemory[0] = 32'b0010000000001000000000000000100000;
    //addi $t0, $zero, 32
    Imemory[1] = 32'b0010000000001001000000000000110111;
    //addi $t1, $zero, 55
    Imemory[2] = 32'b0000000010000100110000000000100100;
    //and $s0, $t0, $t1
    Imemory[3] = 32'b0000000010000100110000000000100101;
    //or $s0, $t0, $t1
    Imemory[4] = 32'b10101100000010000000000000000000100;
    //sw $s0, 4($zero)
    Imemory[5] = 32'b101011000000100000000000000000001000;
    //sw $t0, 8($zero)
    Imemory[6] = 32'b0000000010000100110001000000100000;
    //add $s1, $t0, $t1

```

```
Imemory[7] = 32'b000000001000010011001000000100010;  
//sub $s2, $t0, $t1  
Imemory[8] = 32'b000100100011001000000000000001001;  
//beq $s1, $s2, error0  
Imemory[9] = 32'b100011000001000100000000000000100;  
//lw $s1, 4($zero)  
Imemory[10]= 32'b0011001000110010000000000001001000;  
//andi $s2, $s1, 48  
Imemory[11] =32'b000100100011001000000000000001001;  
//beq $s1, $s2, error1  
Imemory[12] =32'b100011000001001100000000000001000;  
//lw $s3, 8($zero)  
Imemory[13] =32'b000100100001001100000000000001010;  
//beq $s0, $s3, error2  
Imemory[14] =32'b000000010010100011010000000101010;  
//slt $s4, $s2, $s1 (Last)  
Imemory[15] =32'b000100101000000000000000000001111;  
//beq $s4, $0, EXIT  
Imemory[16] =32'b000000010001000001001000000100000;  
//add $s2, $s1, $0  
Imemory[17] =32'b000010000000000000000000000001110;  
//j Last  
Imemory[18] =32'b001000000000100000000000000000000;  
//addi $t0, $0, 0(error0)  
Imemory[19] =32'b001000000000100100000000000000000;  
//addi $t1, $0, 0  
Imemory[20] =32'b000010000000000000000000000001111;  
//j EXIT  
Imemory[21] =32'b001000000000100000000000000000001;  
//addi $t0, $0, 1(error1)  
Imemory[22] =32'b001000000000100100000000000000001;  
//addi $t1, $0, 1  
Imemory[23] =32'b000010000000000000000000000001111;  
//j EXIT  
Imemory[24] =32'b001000000000100000000000000000010;  
//addi $t0, $0, 2(error2)  
Imemory[25] =32'b001000000000100100000000000000010;  
//addi $t1, $0, 2  
Imemory[26] =32'b000010000000000000000000000001111;  
//j EXIT  
Imemory[27] =32'b001000000000100000000000000000011;
```



```
//addi $t0, $0, 3(error3)
Imemory[28] = 32'b00100000000010010000000000000011;
//addi $t1, $0, 3
Imemory[29] = 32'b00001000000000000000000000001111;
//j EXIT
end
endmodule
```

| reset | Read address | PC out |
|-------|--------------------|--|
| 1 | 32'b0 | 32'b0010000000001000000000000000100000 |
| 0 | 32'b0 | 32'b0010000000001000000000000000100000 |
| 0 | 32'b0000..... 0011 | 32'b0000000010000100110000000000100101 |
| 0 | 32'b00000111 | 32'b0000000010000100110010000000100010 |

III.4.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

```
module lab4_ex4_v2(SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    output[0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5;
    wire[31:0] w_out_instruction;
```

```
    assign LEDR[15:0] = SW[17] ? w_out_instruction[31:16] :
w_out_instruction[15:0];
```

```
    Instruction_Memory (.read_address(SW[5:0]),
.instruction(w_out_instruction));
```

```
endmodule
```


```
module Instruction_Memory (read_address, instruction);
    input [7:0] read_address;
    output [31:0] instruction;
    reg [31:0] Imemory [63:0];
    assign instruction=Imemory[read_address];
    initial begin
    Imemory[0] = 32'b0010000000001000000000000000100000;
    //addi $t0, $zero, 32
```

```
Imemory[1] = 32'b00100000000010010000000000110111;  
//addi $t1, $zero, 55  
Imemory[2] = 32'b00000001000010011000000000100100;  
//and $s0, $t0, $t1  
Imemory[3] = 32'b00000001000010011000000000100101;  
//or $s0, $t0, $t1  
Imemory[4] = 32'b10101100000100000000000000000100;  
//sw $s0, 4($zero)  
Imemory[5] = 32'b10101100000010000000000000000100;  
//sw $t0, 8($zero)  
Imemory[6] = 32'b00000001000010011000100000100000;  
//add $s1, $t0, $t1  
Imemory[7] = 32'b00000001000010011001000000100010;  
//sub $s2, $t0, $t1  
Imemory[8] = 32'b00010010001100100000000000000100;  
//beq $s1, $s2, error0  
Imemory[9] = 32'b10001100000100010000000000000100;  
//lw $s1, 4($zero)  
Imemory[10] = 32'b00110010001100100000000000100100;  
//andi $s2, $s1, 48  
Imemory[11] = 32'b00010010001100100000000000000100;  
//beq $s1, $s2, error1  
Imemory[12] = 32'b10001100000100110000000000000100;  
//lw $s3, 8($zero)  
Imemory[13] = 32'b00010010000100110000000000000100;  
//beq $s0, $s3, error2  
Imemory[14] = 32'b000000010010100011010000000101010;  
//slt $s4, $s2, $s1 (Last)  
Imemory[15] = 32'b000100101000000000000000000001111;  
//beq $s4, $0, EXIT  
Imemory[16] = 32'b000000010001000001001000000100000;  
//add $s2, $s1, $0  
Imemory[17] = 32'b000010000000000000000000000001110;  
//j Last  
Imemory[18] = 32'b001000000000100000000000000000000;  
//addi $t0, $0, 0(error0)  
Imemory[19] = 32'b001000000000100100000000000000000;  
//addi $t1, $0, 0  
Imemory[20] = 32'b000010000000000000000000000001111;  
//j EXIT  
Imemory[21] = 32'b001000000000100000000000000000001;
```

```
//addi $t0, $0, 1(error1)
Imemory[22] =32'b00100000000010010000000000000001;
//addi $t1, $0, 1
Imemory[23] =32'b0000100000000000000000000000011111;
//j EXIT
Imemory[24] =32'b001000000000100000000000000000010;
//addi $t0, $0, 2(error2)
Imemory[25] =32'b001000000000100100000000000000010;
//addi $t1, $0, 2
Imemory[26] =32'b0000100000000000000000000000011111;
//j EXIT
Imemory[27] =32'b001000000000100000000000000000011;
//addi $t0, $0, 3(error3)
Imemory[28] =32'b001000000000100100000000000000011;
//addi $t1, $0, 3
Imemory[29] =32'b0000100000000000000000000000011111;
//j EXIT
end
endmodule
```

III.5 EXPERIMENT NO. 5

III.5.1 AIM: To implement the Instruction memory datapath

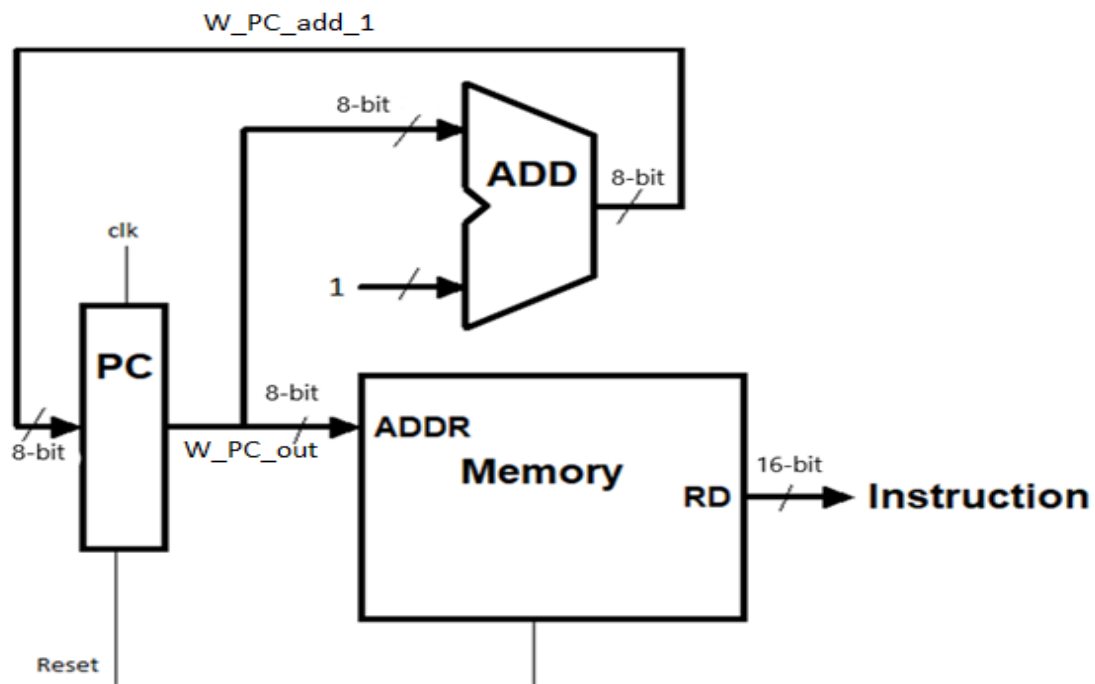

III.5.2 CODE

```
module Instruction_Datapath (clk, reset, Instruction);  
    input clk, reset;  
    output [15:0] Instruction;
```

```
endmodule
```

III.5.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

module

```
lab4_ex5(CLOCK_50,SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,  
HEX6,HEX7);
```

```
    input [17:0]      SW;  
    output[17:0]      LEDR;  
    output[7:0] LEDG;  
    output[7:0]  HEX7,HEX6,HEX5, HEX4, HEX3, HEX2, HEX1, HEX0;  
    input CLOCK_50;  
    wire clk_1Hz;  
    wire [31:0] OUT;  
    clock_divider_1Hz div1 (  
        .clk_in(CLOCK_50),  
        .reset(SW[0]),      // SW[2] = reset  
        .clk_out(clk_1Hz)  
    );
```

```
    Instruction_Datapath DUT (.clk(clk_1Hz),  
    .reset(SW[0]),.instruction_address(LEDG), .Instruction(OUT));
```

```
    wire SEL;  
    assign SEL = SW[17];  
    assign LEDR = SEL ? OUT[15:0] : OUT[31:16];
```

```
    hex7seg h0(OUT[3:0], HEX0);  
    hex7seg h1(OUT[7:4], HEX1);  
    hex7seg h2(OUT[11:8], HEX2);  
    hex7seg h3(OUT[15:12], HEX3);  
    hex7seg h4(OUT[19:16], HEX4);  
    hex7seg h5(OUT[23:20], HEX5);  
    hex7seg h6(OUT[27:24], HEX6);  
    hex7seg h7(OUT[31:28], HEX7);
```

endmodule

```
module Instruction_Datpath (clk, reset, instruction_address, Instruction);
    input clk, reset;
    output [31:0] Instruction;
    output[7:0] instruction_address;

    PC_ADD DUT1(.clk(clk), .reset(reset),
.Instruction_Address(instruction_address));
    MEMORY DUT2(.read_address(instruction_address),
.instruction(Instruction), .reset(reset));
endmodule
```

```
module hex7seg(
    input wire [3:0] hex,
    output reg [7:0] seg
);
    always @(*) begin
        case (hex)
            4'h0: seg = 8'b11000000;
            4'h1: seg = 8'b11111001;
            4'h2: seg = 8'b10100100;
            4'h3: seg = 8'b10110000;
            4'h4: seg = 8'b10011001;
            4'h5: seg = 8'b10010010;
            4'h6: seg = 8'b10000010;
            4'h7: seg = 8'b11111000;
            4'h8: seg = 8'b10000000;
            4'h9: seg = 8'b10010000;
            4'hA: seg = 8'b10001000;
            4'hB: seg = 8'b10000011;
            4'hC: seg = 8'b11000110;
            4'hD: seg = 8'b10100001;
            4'hE: seg = 8'b10000110;
            4'hF: seg = 8'b10001110;
            default: seg = 8'b11111111;
        endcase
    end
endmodule
```



```
module PC_ADD (clk, reset, Instruction_Address);
    input clk, reset;
    output [7:0] Instruction_Address;

    wire [7:0] add_out;

    PC pc1(.clk(clk), .reset(reset), .PC_in(add_out),
    .PC_out(Instruction_Address));
    ADD add1(.input1(Instruction_Address), .input2(8'b0000_0001),
    .out(add_out));
endmodule
```

```
module PC (clk, reset, PC_in, PC_out);
    input clk, reset;
    input [7:0] PC_in;
    output [7:0] PC_out;
    reg [7:0] PC_out;
    always @ (posedge clk or posedge reset)
    begin
        if(reset==1'b1)
            PC_out<=8'b0;
        else
            PC_out<=PC_in;
    end
endmodule
```

```
module ADD(input1, input2, out);

    input [7:0] input1, input2;
    output [7:0] out;

    assign out = input1 + input2;

endmodule
```

```
module MEMORY (read_address, instruction, reset);
    input      reset;
    input [7:0] read_address;
    outputreg [31:0] instruction;
```

reg [31:0] Imemory [1024:0];

always @(*) begin

```
    Imemory[0] = 32'b00100000000010000000000000100000;  
    //addi $t0, $zero, 32  
    Imemory[1] = 32'b00100000000010010000000000110111;  
    //addi $t1, $zero, 55  
    Imemory[2] = 32'b0000000010000100110000000000100100;  
    //and $s0, $t0, $t1  
    Imemory[3] = 32'b0000000010000100110000000000100101;  
    //or $s0, $t0, $t1  
    Imemory[4] = 32'b101011000001000000000000000000100;  
    //sw $s0, 4($zero)  
    Imemory[5] = 32'b1010110000001000000000000000001000;  
    //sw $t0, 8($zero)  
    Imemory[6] = 32'b0000000010000100110001000000100000;  
    //add $s1, $t0, $t1  
    Imemory[7] = 32'b0000000010000100110010000000100010;  
    //sub $s2, $t0, $t1  
    Imemory[8] = 32'b0001001000110010000000000000001001;  
    //beq $s1, $s2, error0  
    Imemory[9] = 32'b100011000001000100000000000000100;  
    //lw $s1, 4($zero)  
    Imemory[10] = 32'b001100100011001000000000001001000;  
    //andi $s2, $s1, 48  
    Imemory[11] = 32'b0001001000110010000000000000001001;  
    //beq $s1, $s2, error1  
    Imemory[12] = 32'b1000110000010011000000000000001000;  
    //lw $s3, 8($zero)  
    Imemory[13] = 32'b0001001000010011000000000000001010;  
    //beq $s0, $s3, error2  
    Imemory[14] = 32'b0000000100101000110100000000101010;  
    //slt $s4, $s2, $s1 (Last)  
    Imemory[15] = 32'b0001001010000000000000000000001111;  
    //beq $s4, $0, EXIT  
    Imemory[16] = 32'b0000000100010000010010000000100000;  
    //add $s2, $s1, $0  
    Imemory[17] = 32'b0000100000000000000000000000001110;  
    //j Last  
    Imemory[18] = 32'b0010000000001000000000000000000000;  
    //addi $t0, $0, 0(error0)
```

```

Imemory[19] = 32'b00100000000010010000000000000000;
//addi $t1, $0, 0
Imemory[20] = 32'b000010000000000000000000000011111;
//j EXIT
Imemory[21] = 32'b00100000000010000000000000000001;
//addi $t0, $0, 1(error1)
Imemory[22] = 32'b00100000000010010000000000000001;
//addi $t1, $0, 1
Imemory[23] = 32'b000010000000000000000000000011111;
//j EXIT
Imemory[24] = 32'b00100000000010000000000000000010;
//addi $t0, $0, 2(error2)
Imemory[25] = 32'b00100000000010010000000000000010;
//addi $t1, $0, 2
Imemory[26] = 32'b000010000000000000000000000011111;
//j EXIT
Imemory[27] = 32'b00100000000010000000000000000011;
//addi $t0, $0, 3(error3)
Imemory[28] = 32'b00100000000010010000000000000011;
//addi $t1, $0, 3
Imemory[29] = 32'b000010000000000000000000000011111;
//j EXIT
end

always @(*) begin
    if(reset)
        instruction = 31'b0;
    else
        instruction = Imemory[read_address];
    end
endmodule

module clock_divider_1Hz (
    input clk_in,
    input reset,
    output reg clk_out
);
    reg [25:0] count;

    always @(posedge clk_in or posedge reset) begin
        if (reset) begin

```


```

count <= 26'd0;
clk_out <= 1'b0;
end else begin
  if (count == 26'd24_999_999) begin
    clk_out <= ~clk_out;
    count <= 26'd0;
  end else begin
    count <= count + 1;
  end
end
end
end
endmodule

```

III.6 EXPERIMENT NO. 6

III.6.1 AIM: To implement the Register File

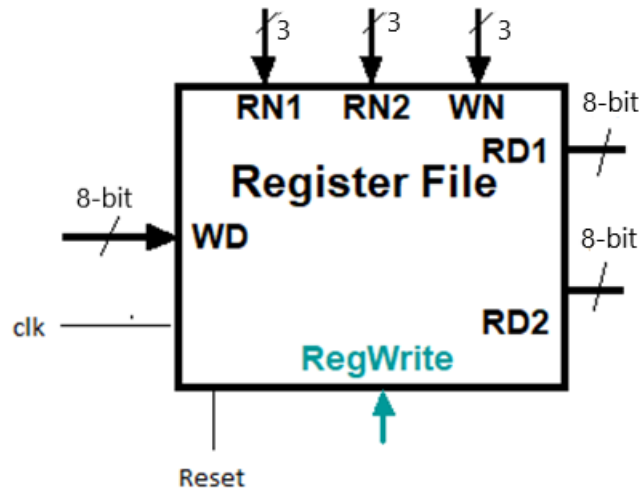

III.6.2 CODE

```

module Register_File (read_addr_1, read_addr_2, write_addr, read_data_1, read_data_2,
write_data, RegWrite, clk, reset);
  input [2:0] read_addr_1, read_addr_2, write_addr;
  input [7:0] write_data;
  input clk, reset, RegWrite;
  output [7:0] read_data_1, read_data_2;

  reg [7:0] Regfile [7:0];
  integer k;

```

```
assign read_data_1 = Regfile[read_addr_1];
```

```
assign read_data_2 = Regfile[read_addr_2];
```

```
always @(posedge clk or posedge reset)
begin
    if (reset==1'b1)
    begin
        for (k=0; k<8; k=k+1)
        begin
            Regfile[k] = 8'b0;
        end
    end

    else if (RegWrite == 1'b1) Regfile[write_addr] = write_data;
end

endmodule
```

| reset | clk | read_addr_1 | read_data_1 | read_addr_2 | read_data_2 | RegWrite | write_addr | write_data |
|-------|-----|-------------|-------------|-------------|-------------|----------|------------|------------|
| 1 | x | x | 32'b0 | x | 32'b0 | x | x | x |
| 0 | ↑ | 32'd3 | 32'b0 | 32'd4 | 32'b0 | 1 | 32'b001 | 32'b0111 |
| 0 | ↑ | 32'd3 | 32'b0 | 32'd4 | 32'b0 | 1 | 32'b010 | 32'b1000 |
| 0 | ↑ | 32'd3 | 32'b0 | 32'd4 | 32'b0 | 1 | 32'b011 | 32'b1001 |
| 0 | ↑ | 32'd3 | 32'b0 | 32'd4 | 32'b0 | 1 | 32'b100 | 32'b1010 |
| 0 | ↑ | 32'd3 | 32'b0 | 32'b00 | 32'b0 | 1 | 32'b101 | 32'b1011 |
| 0 | ↑ | 32'b001 | 32'b0111 | 32'b101 | 32'b1011 | 0 | x | x |
| 0 | ↑ | 32'b011 | 32'b1001 | 32'b100 | 32'b1010 | 0 | x | x |
| 0 | ↑ | 32'b101 | 32'b1011 | 32'b101 | 32'b1011 | 0 | x | x |
| 0 | ↑ | 32'b100 | 32'b1010 | 32'b100 | 32'b1010 | 0 | x | x |

III.6.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT module

```
lab4_ex6_v2(KEY,SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5);
    input[3:0] KEY;
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;
    output[0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5;
```



```
wire [7:0] W_LED_HEX_1_0,W_LED_HEX_3_2;
  assign LEDR = SW;
  Register_File DUT( .read_addr_1(SW[17:15]),
                    .read_addr_2(SW[14:12]),
                    .write_addr(SW[11:9]),
                    .read_data_1(W_LED_HEX_1_0),
                    .read_data_2(W_LED_HEX_3_2),
                    .write_data(SW[8:1]),
                    .RegWrite(SW[0]),
                    .clk(KEY[0]),
                    .reset(KEY[1]));

  HEX_7SEG_DECODE H0(.BIN(W_LED_HEX_1_0[3:0]), .SSD(HEX0));
  HEX_7SEG_DECODE H1(.BIN(W_LED_HEX_1_0[7:4]), .SSD(HEX1));
  HEX_7SEG_DECODE H2(.BIN(W_LED_HEX_3_2[3:0]), .SSD(HEX2));
  HEX_7SEG_DECODE H3(.BIN(W_LED_HEX_3_2[7:4]), .SSD(HEX3));
```

endmodule

```
module HEX_7SEG_DECODE(BIN, SSD);
  input [3:0] BIN;
  output reg [0:6] SSD;
  always begin
    case(BIN)
      0:SSD=7'b0000001;
      1:SSD=7'b1001111;
      2:SSD=7'b0010010;
      3:SSD=7'b0000110;
      4:SSD=7'b1001100;
      5:SSD=7'b0100100;
      6:SSD=7'b0100000;
      7:SSD=7'b0001111;
      8:SSD=7'b0000000;
      9:SSD=7'b0001100;
      10:SSD=7'b0001000;
      11:SSD=7'b1100000;
      12:SSD=7'b0110001;
      13:SSD=7'b1000010;
      14:SSD=7'b0110000;
      15:SSD=7'b0111000;
    endcase
  end
```

```
end
endmodule

module Register_File (read_addr_1, read_addr_2, write_addr, read_data_1,
read_data_2, write_data, RegWrite, clk, reset);
    input [2:0] read_addr_1, read_addr_2, write_addr;
    input [7:0] write_data;
    input clk, reset, RegWrite;
    output [7:0] read_data_1, read_data_2;

    reg [7:0] Regfile [7:0];
    integer k;

    assign read_data_1 = Regfile[read_addr_1];

    assign read_data_2 = Regfile[read_addr_2];


    always @(posedge clk or negedge reset)
    begin
        if (reset==1'b0)
        begin
            for (k=0; k<8; k=k+1)
            begin
                Regfile[k] = 8'b0;
            end
        end

        else if (RegWrite == 1'b1) Regfile[write_addr] = write_data;
    end

endmodule
```

III.7 EXPERIMENT NO. 7

III.7.1 AIM: To implement the ALU

 

III.7.2 CODE

```

module alu(
    input [2:0] alufn,
    input [7:0] ra,
    input [7:0] rb_or_imm,
    output reg [7:0] aluout,
    output reg zero);

    parameter    ALU_OP_ADD      = 3'b000,
                  ALU_OP_SUB      = 3'b001,
                  ALU_OP_AND      = 3'b010,
                  ALU_OP_OR       = 3'b011,
                  ALU_OP_NOT_A    = 3'b100,
                  ALU_OP_LW       = 3'b101,
                  ALU_OP_SW       = 3'b110,
                  ALU_OP_BEQ      = 3'b111;

    always @(*)
    begin
        case(alufn)
            ALU_OP_ADD      : aluout = ra + rb_or_imm;
            ALU_OP_SUB      : aluout = ra - rb_or_imm;
            ALU_OP_AND      : aluout = ra & rb_or_imm;
            ALU_OP_OR       : aluout = ra | rb_or_imm;
            ALU_OP_NOT_A    : aluout = ~ ra;
            ALU_OP_LW       : aluout = ra + rb_or_imm;
            ALU_OP_SW       : aluout = ra + rb_or_imm;
            ALU_OP_BEQ      : begin
                                zero = (ra==rb_or_imm)?1'b1:1'b0;
                                aluout = ra - rb_or_imm;
                            end
        endcase
    end
end

```


endmodule

| alufn | ra | rb or imm | aluout | zero |
|--------|----------|-----------|----------|------|
| 3'b000 | 32'd8 | 32'd2 | 32'd10 | 0 |
| 3'b001 | 32'd8 | 32'd2 | 32'd6 | 0 |
| 3'b010 | 32'b1000 | 32'b0010 | 32'b0000 | 0 |
| 3'b011 | 32'b1000 | 32'b0010 | 32'b1010 | 0 |
| 3'b100 | 32'b1000 | 32'd2 | 32'b0111 | 0 |
| 3'b101 | 32'd8 | 32'd2 | 32'd10 | 0 |
| 3'b110 | 32'd8 | 32'd2 | 32'd10 | 0 |
| 3'b111 | 32'd8 | 32'd2 | 32'd6 | 0 |
| 3'b111 | 32'd8 | 32'd8 | 32'd0 | 1 |

III.7.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

```

module lab4_ex7(LEDG, LEDR, SW);
    input [17:0] SW;
    output[17:0] LEDR;
    output[7:0] LEDG;
    assign LEDR =SW;


    alu(.alufn(SW[17:15]),
        .ra(SW[6:0]),
        .rb_or_imm(SW[14:7]),
        .aluout(LEDG[6:0]),
        .zero(LEDG[7]));

```

endmodule

III.8 EXPERIMENT NO. 8

III.8.1 AIM: To implement the 32 bit RAM

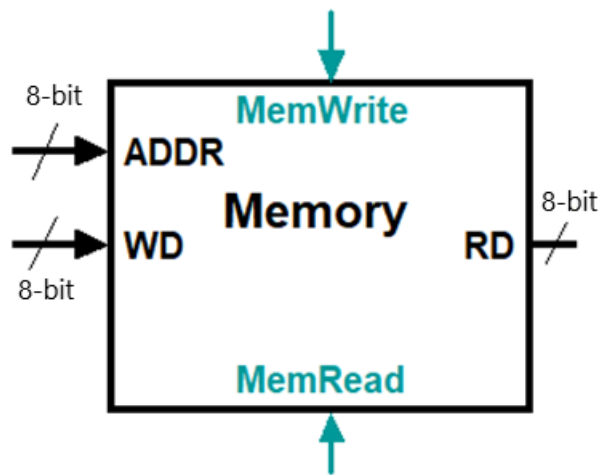

III.8.2 CODE

```
module Data_Memory (addr, write_data, read_data, clk, reset, MemRead, MemWrite);
    input [7:0] addr;
    input [7:0] write_data;
    output [7:0] read_data;
    input clk, reset, MemRead, MemWrite;
    reg [7:0] DMemory [7:0];
    integer k;
    assign read_data = (MemRead) ? DMemory[addr] : 8'bx;
```

```
    always @(posedge clk or posedge reset)
    begin
        if (reset == 1'b1)
            begin
                for (k=0; k<8; k=k+1)
                    begin
                        DMemory[k] = 8'b0;
                    end
            end
        else
            if (MemWrite) DMemory[addr] = write_data;
        end
    end
endmodule
```

III.8.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

```

module lab4_ex8(SW,LEDG,LEDR);
    input [17:0] SW;
    output[17:0] LEDR;
    output[7:0] LEDG;
    assign LEDR = SW;


    Data_Memory (    .addr(SW[6:0]),
                    .write_data(SW[13:7]),
                    .read_data(LEDG[6:0]),
                    .clk(SW[17]),
                    .reset(SW[16]),
                    .MemRead(SW[15]),
                    .MemWrite(SW[14]));

Endmodule

```

III.9 EXPERIMENT NO. 9

III.9.1 AIM: To implement Multiplexer

 

III.9.2 CODE

```

module Mux_N_bit (in0, in1, mux_out, select);
    parameter N = 32;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;

```

```
input control;
assign mux_out = select? in1: in0 ;
endmodule
```

III.9.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT


```
module lab4_ex9(SW, LEDR, LEDG);
    input[17:0] SW;
    output[7:0] LEDG;
    output[17:0] LEDR;

    Mux_N_bit (.in0(SW[7:0]), .in1(SW[15:8]), .mux_out(LEDG[7:0]), .select(SW[16]));
endmodule
```

```
module Mux_N_bit (in0, in1, mux_out, select);
    parameter N = 8;
    input select;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    assign mux_out = select? in1: in0 ;
endmodule
```

III.10 EXPERIMENT NO. 10

III.10.1 AIM: To implement Sign_Extension

 

III.10.2 CODE

```
module Sign_Extension (sign_in, sign_out);
    input [15:0] sign_in;
    output [31:0] sign_out;
    assign sign_out[15:0]=sign_in[15:0];
endmodule
```

```
    assign sign_out[31:16]=sign_in[15]?{16{1'b1}}:16'b0;  
endmodule
```

III.10.3 LAB ASSIGNMENT

1. Write testbenches to verify above module and attach waveforms.
2. Write the Top level module to implement this module in FPGA KIT

```
module lab4_ex10(SW, LEDR,LEDG);  
    input[17:0] SW;  
    output[7:0] LEDG;  
    output[17:0] LEDR;
```

```
        Sign_Extension (.sign_in(SW[4:0]), .sign_out(LEDG[7:0]));  
endmodule
```

```
module Sign_Extension (sign_in, sign_out);  
    input [4:0] sign_in;  
    output [7:0] sign_out;  
    assign sign_out[4:0]=sign_in[4:0];  
    assign sign_out[7:5]=sign_in[4]?{3{1'b1}}:3'b0;  
endmodule
```