



DIGITAL SYSTEM DESIGN LABORATORY

REPORT LAB 5

SINGLE CYCLE MICROPROCESSOR DATAPATH DESIGN

Name: Bùi Gia Bảo
ID: ITITIU22019

I. LAB OBJECTIVES

This Lab experiments are intended to design and test a Single Cycle Microprocessor

II. DESCRIPTION

Single Cycle Microprocessor datapath to be implemented is in figure 2.1.

 


Figure 2.1: Single Cycle Microprocessor DataPath

III. LAB PROCEDURE

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To understand and write the assembly code using MIPS Instruction set

register number of MIPS compiler conventions

Name	Register number	Usage
\$zero	0	the constant value 0
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved (by callee)
\$t8-\$t9	24-25	more temporaries
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address

MIPS Assembly Language Sumarize:

MIPS assembly language				
Category	Instruction	Example	Meaning	Comments
Arithmetic	add	add \$s1, \$s2, \$s3	$\$s1 = \$s2 + \$s3$	Three operands; data in registers
	subtract	sub \$s1, \$s2, \$s3	$\$s1 = \$s2 - \$s3$	Three operands; data in registers
	add immediate	addi \$s1, \$s2, 100	$\$s1 = \$s2 + 100$	Used to add constants
Data transfer	load word	lw \$s1, 100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Word from memory to register
	store word	sw \$s1, 100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Word from register to memory
	load byte	lb \$s1, 100(\$s2)	$\$s1 = \text{Memory}[\$s2 + 100]$	Byte from memory to register
	store byte	sb \$s1, 100(\$s2)	$\text{Memory}[\$s2 + 100] = \$s1$	Byte from register to memory
	load upper immediate	lui \$s1, 100	$\$s1 = 100 * 2^{16}$	Loads constant in upper 16 bits
Conditional branch	branch on equal	beq \$s1, \$s2, 25	if ($\$s1 == \$s2$) go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1, \$s2, 25	if ($\$s1 != \$s2$) go to PC + 4 + 100	Not equal test; PC-relative
	set on less than	slt \$s1, \$s2, \$s3	if ($\$s2 < \$s3$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than; for beq, bne
	set less than immediate	slti \$s1, \$s2, 100	if ($\$s2 < 100$) $\$s1 = 1$; else $\$s1 = 0$	Compare less than constant
Uncondi- tional jump	jump	j 2500	go to 10000	Jump to target address
	jump register	jr \$ra	go to \$ra	For sw itch, procedure return
	jump and link	jal 2500	$\$ra = \text{PC} + 4$; go to 10000	For procedure call

Operation code (Op code) summarize:


Op	Opcode name	Value
000000	R-format	Rformat1
000010	jmp	JUMP1
000100	beq	BEQ1
100011	lw	Mem1
101011	sw	Mem1

ALU opcode and Function

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Instruction Formats

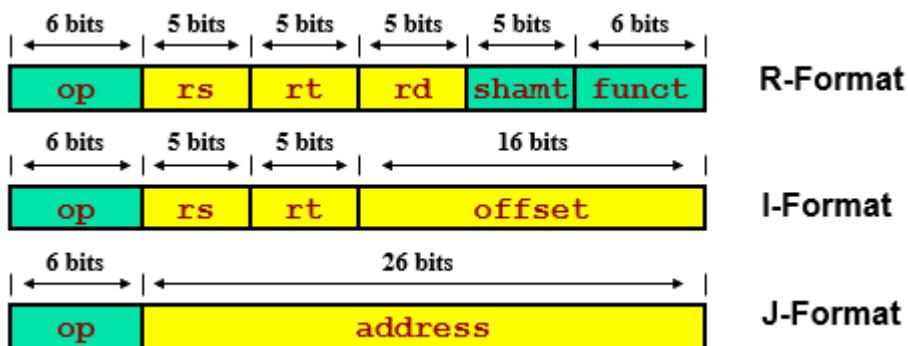

III.1.2 CODE

a) Assembly Code sample 1:

<u>Instruction</u>	<u>Meaning</u>
addi \$s0, \$zero, 33	load immediate value 33 to register \$s0
addi \$s1, \$zero, 66	load immediate value 66 to register \$s1
add \$s2, \$s0, \$s1	$\$s2 = \$s0 + \$s1$
sub \$s3, \$s1, \$s0	$\$s1 = \$s1 - \$s0$
sw \$s3, 10(\$s2)	Memory[\$s2+10] = \$s3
lw \$s1, 10(\$s2)	$\$s1 = \text{Memory}[\$s2+10]$

b) Assembly Code sample 2:

Assume the code start from address PC=0x00000000, one instruction is store in one memory location.

<u>Instruction</u>	<u>Meaning</u>
addi \$s2, \$zero, 55	load immediate value 55 to register \$s2
addi \$s3, \$zero, 22	load immediate value 22 to register \$s3
addi \$s5, \$zero, 33	load immediate value 55 to register \$s3
add \$s4, \$s2, \$s3	$\$s4 = \$s2 + \$s3$
sub \$s1, \$s2, \$s3	$\$s1 = \$s2 - \$s3$
sw \$s1, 100(\$s2)	Memory[\$s2+100] = \$s1
lw \$s1, 100(\$s2)	$\$s1 = \text{Memory}[\$s2+100]$
bne \$s1, \$s5, End	Next instr. is at End if $\$s4 \neq \$s5$
addi \$s6, \$zero, 10	load immediate value 10 to register \$s6
beq \$s4, \$s5, End	Next instr. is at End if $\$s4 = \$s5$
addi \$s6, \$zero, 20	load immediate value 20 to register \$s6
End: j End	jump Here

III.1.3 LAB ASSIGNMENT

- Compile the Assembly **Assembly Code sample 1** into machine code (decimal code and binary code)
- Explain briefly the meaning of **Assembly Code sample 1**
- Compile the Assembly **Assembly Code sample 2** into machine code (decimal code and binary code)
- Explain briefly the meaning of **Assembly Code sample 2**

III.2 EXPERIMENT NO. 2

III.2.1 AIM: To implement R-Type Datapath

Name	Register number	Usage
\$zero	0	the constant value 0
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved (by callee)
\$t8-\$t9	24-25	more temporaries
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address

Given the assembly code

addi \$s1, \$zero, 33 load immediate value 33 to register \$s0

addi \$s2, \$zero, 66 load immediate value 66 to register \$s1

add \$s0, \$s1, \$s2 \$s0 = \$s1 + \$s2

Translate into Machine code:

Assembly Code

add \$s0, \$s1, \$s2

Field Values

op	rs	rt	rd	shamt	funct
0	17	18	16	0	32

Machine Code

op	rs	rt	rd	shamt	funct
000000	10001	10010	10000	00000	100000

Modify the code register file:

- Assign initial value of the register 17=33 (\$s1=33)
- Assign initial value of the register 18=66 (\$s2=66)


Instruction



add rd, rs, rt


ADD \$s0, \$s1, s2

R[rd] <- R[rs] + R[rt];

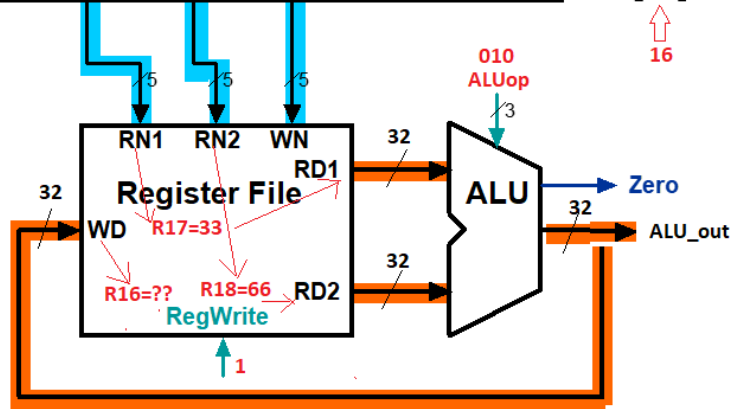

Name	Register number
\$zero	0
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$gp	28
\$sp	29
\$fp	30
\$ra	31


Instruction

 

SUB rd, rs, rt

Sub \$s0, \$s1, s2

R[rd] <- R[rs] - R[rt];

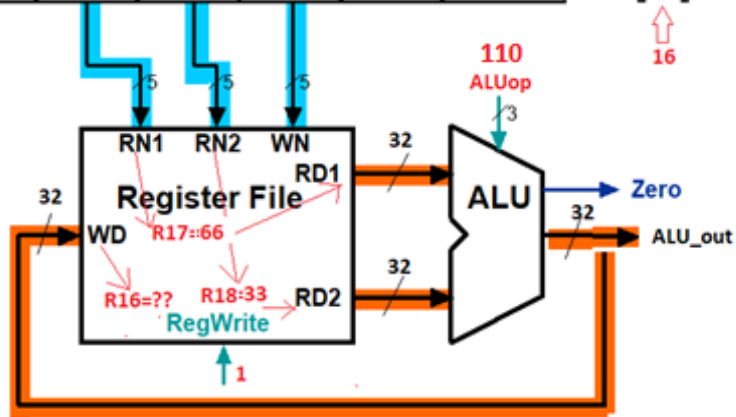

Name	Register number
\$zero	0
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$gp	28
\$sp	29
\$fp	30
\$ra	31

III.2.2 CODE

module

lab5_ex2(KEY,SW,LEDG,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7);

input[3:0] KEY;

input [17:0] SW;

output[17:0] LEDR;

output[7:0] LEDG;

output [0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7;

wire [31:0] w_hex;

assign LEDR =SW;

wire [2:0] op;

```
//assign op = SW[17] ? 3'b010 : 3'b110;
```

```
DatapathR_Type_Add(.rs(SW[14:10]), .rt(SW[9:5]), .rd(SW[4:0]),  
                  .ALUop(SW[17:15]),  
                  .Zero(LEDG[7]),  
                  .ALU_out(w_hex),  
                  .reset(KEY[0]),  
                  .clk(KEY[1]),  
                  .regWrite(1'b1));
```

```
HEX_7SEG_DECODE H0(.BIN(w_hex[3:0]), .SSD(HEX0));  
HEX_7SEG_DECODE H1(.BIN(w_hex[7:4]), .SSD(HEX1));  
HEX_7SEG_DECODE H2(.BIN(w_hex[11:8]), .SSD(HEX2));  
HEX_7SEG_DECODE H3(.BIN(w_hex[15:12]), .SSD(HEX3));  
HEX_7SEG_DECODE H4(.BIN(w_hex[19:16]), .SSD(HEX4));  
HEX_7SEG_DECODE H5(.BIN(w_hex[23:20]), .SSD(HEX5));  
HEX_7SEG_DECODE H6(.BIN(w_hex[27:24]), .SSD(HEX6));  
HEX_7SEG_DECODE H7(.BIN(w_hex[31:28]), .SSD(HEX7));
```

```
endmodule
```

```
module DatapathR_Type_Add(rs, rt, rd,ALUop, Zero ,ALU_out, reset, clk,  
regWrite);
```

```
    input[4:0] rs, rt, rd;  
    input[2:0] ALUop;  
    output Zero;  
    output[31:0] ALU_out;  
    wire[31:0] w_rd_1, w_rd_2, w_rd_11, w_rd_22;  
    input clk;  
    input reset;  
    input regWrite;
```

```
    assign w_rd_11 = 32'h0000_0003;  
    assign w_rd_22 = 32'h0000_0001;
```

```
    Register_File ( .read_addr_1(rs),  
                   .read_addr_2(rt),  
                   .write_addr(rd),  
                   .read_data_1(w_rd_1),  
                   .read_data_2(w_rd_2),
```



```
.write_data(ALU_out),  
.RegWrite(regWrite),  
.clk(clk),  
.reset(reset));
```

```
alu( .alufn(ALUOp),  
     .ra(w_rd_1),  
     .rb_or_imm(w_rd_2),  
     .aluout(ALU_out),  
     .zero(Zero));
```

```
endmodule
```

```
module HEX_7SEG_DECODE(BIN, SSD);  
  input [3:0] BIN;  
  output reg [0:6] SSD;  
  always begin  
    case(BIN)  
      0:SSD=7'b0000001;  
      1:SSD=7'b1001111;  
      2:SSD=7'b0010010;  
      3:SSD=7'b0000110;  
      4:SSD=7'b1001100;  
      5:SSD=7'b0100100;  
      6:SSD=7'b0100000;  
      7:SSD=7'b0001111;  
      8:SSD=7'b0000000;  
      9:SSD=7'b0001100;  
      10:SSD=7'b0001000;  
      11:SSD=7'b1100000;  
      12:SSD=7'b0110001;  
      13:SSD=7'b1000010;  
      14:SSD=7'b0110000;  
      15:SSD=7'b0111000;  
    endcase  
  end  
endmodule
```



```
module Register_File (read_addr_1, read_addr_2, write_addr, read_data_1,
read_data_2, write_data, RegWrite, clk, reset);
    input [4:0] read_addr_1, read_addr_2, write_addr;
    input [31:0] write_data;
    input clk, reset, RegWrite;
    output [31:0] read_data_1, read_data_2;

    reg [31:0] Regfile [31:0];
    integer k;

    //assign Regfile[17] = 32'h33;
    //assign Regfile[18] = 32'h66;

    assign read_data_1 = RegWrite ? Regfile[read_addr_1] : 32'b0;

    assign read_data_2 = RegWrite ? Regfile[read_addr_2] : 32'b0;

    always @(posedge clk or negedge reset)
    begin
        if (reset==1'b0)
        begin
            for (k=0; k<32; k=k+1)
            begin
                Regfile[k] = 32'b0;
            end
        end

        else begin
            if (RegWrite == 1'b1) Regfile[write_addr] = write_data;
            Regfile[17] = 32'h33;
            Regfile[18] = 32'h66;
        end

    end

endmodule

module alu(
    input [2:0] alufn,
```


```
input [31:0] ra,
input [31:0] rb_or_imm,
output reg [31:0] aluout,
output wire zero);

parameter  ALU_OP_ADD    = 3'b010,
            ALU_OP_SUB    = 3'b110,
            ALU_OP_AND    = 3'b000,
            ALU_OP_OR     = 3'b001,
            ALU_OP_NOT_A  = 3'b100,
            ALU_OP_LW     = 3'b101,
            ALU_OP_SW     = 3'b011,
            ALU_OP_BEQ    = 3'b111;

assign zero = ((alufn == ALU_OP_BEQ) && (ra==rb_or_imm))?1'b1:1'b0;
always @(*)
begin
    case(alufn)
        ALU_OP_ADD    : aluout = ra + rb_or_imm;
        ALU_OP_SUB    : aluout = ra - rb_or_imm;
        ALU_OP_AND    : aluout = ra & rb_or_imm;
        ALU_OP_OR     : aluout = ra | rb_or_imm;
        ALU_OP_NOT_A  : aluout = ~ ra;
        ALU_OP_LW     : aluout = ra + rb_or_imm;
        ALU_OP_SW     : aluout = ra + rb_or_imm;
        ALU_OP_BEQ    : aluout = ra - rb_or_imm;
    endcase
end
endmodule
```

III.3 EXPERIMENT NO. 3

III.3.1 AIM: To implement SW I-Type Instruction Datapath

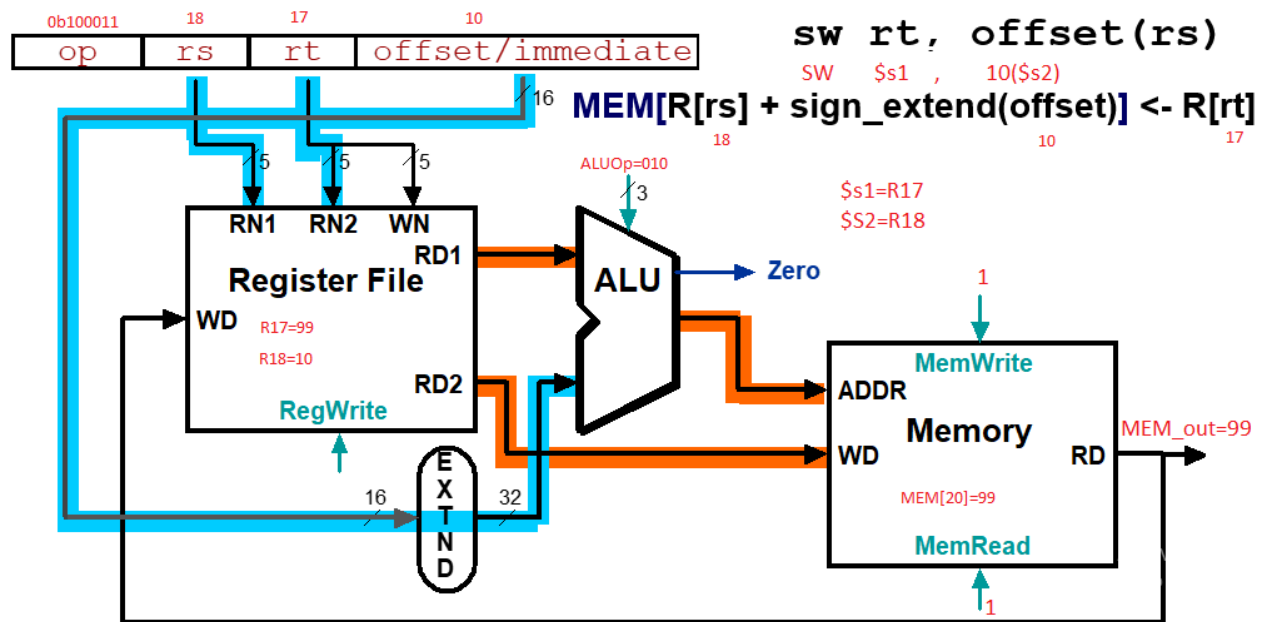

III.3.2 CODE

```
module lab5_ex3(KEY,SW,LEDG,LEDR,HEX0,HEX1,HEX2);
```

```
    input[3:0] KEY;
```

```
    input [17:0]      SW;
```

```
    output[17:0]      LEDR;
```

```
    output[7:0] LEDG;
```

```
    output [0:6] HEX0,HEX1,HEX2;
```

```
    wire [7:0] w_hex,w_hex_2;
```

```
    assign LEDR =SW;
```

```
    //assign op = SW[17] ? 3'b010 : 3'b110;
```

```
    SW_datapath (    .rs(SW[2:0]),
                    .rt(SW[5:3]),
                    .offset(SW[10:6]),
                    .ALUOp(SW[13:11]),
                    .MemWrite(SW[14]),
                    .MemRead(SW[15]),
```

```
.Mem_out(w_hex),  
.reset(SW[17]),  
.clk(KEY[1]),  
.regWrite(1'b1));
```

```
HEX_7SEG_DECODE H0(.BIN(w_hex[3:0]), .SSD(HEX0));  
HEX_7SEG_DECODE H1(.BIN(w_hex[7:4]), .SSD(HEX1));
```

```
endmodule
```

```
module SW_datapath (rs, rt, offset,ALUop,MemWrite,MemRead,Mem_out, reset,  
clk, regWrite);
```

```
input[2:0] rs, rt;  
input[2:0] ALUop;  
input[4:0] offset;  
input MemWrite, MemRead;  
output[7:0] Mem_out;
```

```
wire[7:0] ALU_out;  
wire[7:0] w_rd_1, w_rd_2, w_rd_11, w_rd_22;  
wire[7:0] w_mrd, w_offset_ext;
```

```
input clk;  
input reset;  
input regWrite;
```

```
Register_File (    .read_addr_1(rs),
                  .read_addr_2(rt),
                  .write_addr(rt),
                  .read_data_1(w_rd_1),
                  .read_data_2(w_rd_2),
                  .write_data(8'b00000000),
                  .RegWrite(regWrite),
                  .clk(clk),
                  .reset(reset));

alu(    .alufn(ALUOp),
      .ra(w_rd_1),
      .rb_or_imm(w_offset_ext),
      .aluout(ALU_out),
      .zero(Zero));

Data_Memory (    .addr(ALU_out),
                .write_data(w_rd_2),
                .read_data(Mem_out),
                .clk(clk),
                .reset(reset),
                .MemRead(MemRead),
                .MemWrite(MemWrite));

Sign_Extension (.sign_in(offset), .sign_out(w_offset_ext));
```

endmodule

```
module HEX_7SEG_DECODE(BIN, SSD);
```

```
  input [3:0] BIN;
```

```
  output reg [0:6] SSD;
```

```
  always begin
```

```
    case(BIN)
```

```
      0:SSD=7'b0000001;
```

```
      1:SSD=7'b1001111;
```

```
      2:SSD=7'b0010010;
```

```
      3:SSD=7'b0000110;
```

```
      4:SSD=7'b1001100;
```

```
      5:SSD=7'b0100100;
```

```
      6:SSD=7'b0100000;
```

```
      7:SSD=7'b0001111;
```

```
      8:SSD=7'b0000000;
```

```
      9:SSD=7'b0001100;
```

```
     10:SSD=7'b0001000;
```

```
     11:SSD=7'b1100000;
```

```
     12:SSD=7'b0110001;
```

```
     13:SSD=7'b1000010;
```

```
     14:SSD=7'b0110000;
```

```
     15:SSD=7'b0111000;
```

```
    endcase
```

```
  end
```

```
endmodule
```

```
module Register_File (read_addr_1, read_addr_2, write_addr, read_data_1,
read_data_2, write_data, RegWrite, clk, reset);
    input [2:0] read_addr_1, read_addr_2, write_addr;
    input [7:0] write_data;
    input clk, reset, RegWrite;
    output [7:0] read_data_1, read_data_2;

    reg [7:0] Regfile [7:0];
    integer k;

    assign read_data_1 = RegWrite ? Regfile[read_addr_1] : 8'b0;

    assign read_data_2 = RegWrite ? Regfile[read_addr_2] : 8'b0;

    always @(posedge clk or negedge reset)
    begin
        if (reset==1'b0)
        begin
            for (k=0; k<8; k=k+1)
            begin
                Regfile[k] = 8'b0;
            end
        end

        else begin
            if (RegWrite == 1'b1) Regfile[write_addr] = write_data;
            Regfile[3] = 8'h1;
            Regfile[5] = 8'h2;
            Regfile[6] = 8'h3;
            Regfile[4] = 8'h2;
```




end

end

endmodule

```
module alu(
    input [2:0] alufn,
    input [7:0] ra,
    input [7:0] rb_or_imm,
    output reg [7:0] aluout,
    output wire zero);

    parameter  ALU_OP_ADD    = 3'b010,
               ALU_OP_SUB    = 3'b110,
               ALU_OP_AND    = 3'b000,
               ALU_OP_OR     = 3'b001,
               ALU_OP_NOT_A  = 3'b100,
               ALU_OP_LW     = 3'b101,
               ALU_OP_SW     = 3'b011,
               ALU_OP_BEQ    = 3'b111;

    assign zero = ((alufn == ALU_OP_BEQ) && (ra==rb_or_imm))?1'b1:1'b0;
    always @(*)
    begin
        case(alufn)
            ALU_OP_ADD    : aluout = ra + rb_or_imm;
```

```
        ALU_OP_SUB      : aluout = ra - rb_or_imm;
        ALU_OP_AND      : aluout = ra & rb_or_imm;
        ALU_OP_OR       : aluout = ra | rb_or_imm;
        ALU_OP_NOT_A    : aluout = ~ ra;
        ALU_OP_LW       : aluout = ra + rb_or_imm;
        ALU_OP_SW       : aluout = ra + rb_or_imm;
        ALU_OP_BEQ      : aluout = ra - rb_or_imm;
    endcase

end

endmodule

module Data_Memory (addr, write_data, read_data, clk, reset, MemRead,
MemWrite);
    input [7:0] addr;
    input [7:0] write_data;
    output [7:0] read_data;
    input clk, reset, MemRead, MemWrite;
    reg [7:0] DMemory [7:0];
    integer k;
    assign read_data = (MemRead && ~MemWrite) ? DMemory[addr] : 8'bx;

    always @(posedge clk or negedge reset)
    begin
        if (reset == 1'b0)
            begin
                for (k=0; k<8; k=k+1)
                    begin
                        DMemory[k] = 8'b0;
                    end
            end
        else

```

```

        if (MemWrite) DMemory[addr] = write_data;

    end

endmodule

```


```

module Sign_Extension (sign_in, sign_out);
    input [4:0] sign_in;
    output [7:0] sign_out;
    assign sign_out[4:0]=sign_in[4:0];
    assign sign_out[7:5]=sign_in[4]?{3{1'b1}}:3'b0;
endmodule

```

III.4 EXPERIMENT NO. 4

III.4.1 AIM: To implement LW I-Type Instruction Datapath

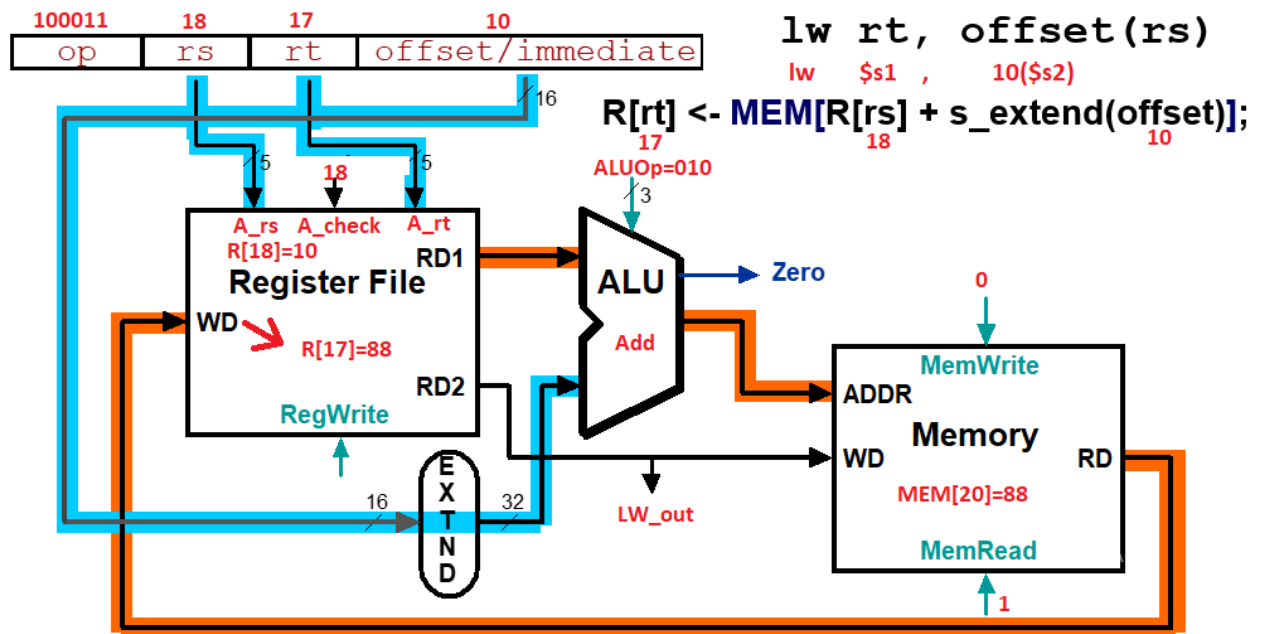

III.4.2 CODE

```

module lab5_ex4(KEY,SW,LEDG,LEDR,HEX0,HEX1,HEX2);
    input[3:0] KEY;
    input [17:0] SW;
    output[17:0] LEDR;
    output[7:0] LEDG;

    output [0:6] HEX0,HEX1,HEX2;

```

```
wire [7:0] w_hex,w_hex_2;  
assign LEDR =SW;
```

```
LW_datapath (    .rs(SW[2:0]),  
                .rt(SW[5:3]),  
                .offset(SW[10:6]),  
                .ALUop(SW[13:11]),  
                .MemWrite(SW[14]),  
                .MemRead(SW[15]),  
                .LW_out(w_hex),  
                .reset(SW[17]),  
                .clk(KEY[1]),  
                .regWrite(1'b1));
```

```
HEX_7SEG_DECODE H0(.BIN(w_hex[3:0]), .SSD(HEX0));  
HEX_7SEG_DECODE H1(.BIN(w_hex[7:4]), .SSD(HEX1));
```

```
endmodule
```

```
module LW_datapath (rs, rt, offset, ALUop,MemWrite,MemRead, LW_out, reset,  
clk, regWrite);
```

```
    input[2:0] rs, rt;  
    input[2:0] ALUop;  
    input[4:0] offset;  
    input MemWrite, MemRead;  
    output[7:0] LW_out;
```

```
    wire[7:0] ALU_out;  
    wire[7:0] w_rd_1, w_rd_2, w_rd_11, w_rd_22;  
    wire[7:0] w_mrd, w_offset_ext;
```

```
    input clk;  
    input reset;  
    input regWrite;
```

```
Register_File (    .read_addr_1(rs),
                  .read_addr_2(rt),
                  .write_addr(rt),
                  .read_data_1(w_rd_1),
                  .read_data_2(w_rd_2),
                  .write_data(LW_out),
                  .RegWrite(regWrite),
                  .clk(clk),
                  .reset(reset));

alu(    .alufn(ALUop),
      .ra(w_rd_1),
      .rb_or_imm(w_offset_ext),
      .aluout(ALU_out),
      .zero(Zero));

Data_Memory (    .addr(ALU_out),
                .write_data(8'b00000000),
                .read_data(LW_out),
                .clk(clk),
                .reset(reset),
                .MemRead(MemRead),
                .MemWrite(MemWrite));

Sign_Extension (.sign_in(offset), .sign_out(w_offset_ext));

endmodule
```

```
module HEX_7SEG_DECODE(BIN, SSD);
input [3:0] BIN;
output reg [0:6] SSD;
always begin
case(BIN)
0:SSD=7'b00000001;
```



```
1:SSD=7'b1001111;  
2:SSD=7'b0010010;  
3:SSD=7'b0000110;  
4:SSD=7'b1001100;  
5:SSD=7'b0100100;  
6:SSD=7'b0100000;  
7:SSD=7'b0001111;  
8:SSD=7'b0000000;  
9:SSD=7'b0001100;  
10:SSD=7'b0001000;  
11:SSD=7'b1100000;  
12:SSD=7'b0110001;  
13:SSD=7'b1000010;  
14:SSD=7'b0110000;  
15:SSD=7'b0111000;  
endcase  
end  
endmodule  
  
module Register_File (read_addr_1, read_addr_2, write_addr, read_data_1,  
read_data_2, write_data, RegWrite, clk, reset);  
    input [2:0] read_addr_1, read_addr_2, write_addr;  
    input [7:0] write_data;  
    input clk, reset, RegWrite;  
    output [7:0] read_data_1, read_data_2;  
  
    reg [7:0] Regfile [7:0];  
    integer k;  
  
    assign read_data_1 = RegWrite ? Regfile[read_addr_1] : 8'b0;  
  
    assign read_data_2 = RegWrite ? Regfile[read_addr_2] : 8'b0;  
  
    always @(posedge clk or negedge reset)  
    begin  
        if (reset==1'b0)  
        begin  
            for (k=0; k<8; k=k+1)  
            begin  
                Regfile[k] = 8'b0;  
            end  
        end  
    end
```

```
        end
    end

    else begin
        if (RegWrite == 1'b1) Regfile[write_addr] = write_data;

        end

    end

end

endmodule


module alu(
    input [2:0] alufn,
    input [7:0] ra,
    input [7:0] rb_or_imm,
    output reg [7:0] aluout,
    output wire zero);

    parameter  ALU_OP_ADD    = 3'b010,
               ALU_OP_SUB    = 3'b110,
               ALU_OP_AND    = 3'b000,
               ALU_OP_OR     = 3'b001,
               ALU_OP_NOT_A  = 3'b100,
               ALU_OP_LW     = 3'b101,
               ALU_OP_SW     = 3'b011,
               ALU_OP_BEQ    = 3'b111;

    assign zero = ((alufn == ALU_OP_BEQ) && (ra==rb_or_imm))?1'b1:1'b0;
    always @(*)
    begin
        case(alufn)
            ALU_OP_ADD    : aluout = ra + rb_or_imm;
            ALU_OP_SUB    : aluout = ra - rb_or_imm;
            ALU_OP_AND    : aluout = ra & rb_or_imm;
            ALU_OP_OR     : aluout = ra | rb_or_imm;
            ALU_OP_NOT_A  : aluout = ~ ra;
            ALU_OP_LW     : aluout = ra + rb_or_imm;
```

```

        ALU_OP_SW          : aluout = ra + rb_or_imm;
        ALU_OP_BEQ        : aluout = ra - rb_or_imm;
    endcase
end
endmodule

module Data_Memory (addr, write_data, read_data, clk, reset, MemRead,
MemWrite);
    input [7:0] addr;
    input [7:0] write_data;
    output [7:0] read_data;
    input clk, reset, MemRead, MemWrite;
    reg [7:0] DMemory [7:0];
    integer k;
    assign read_data = (MemRead && ~MemWrite) ? DMemory[addr] : 8'bx;


    always @(posedge clk or negedge reset)
    begin
        if (reset == 1'b0)
            begin
                for (k=0; k<8; k=k+1)
                    begin
                        DMemory[k] = 8'b0;
                    end
            end
        else begin
            if (MemWrite) DMemory[addr] = write_data;
            DMemory[5] = 8'h8;
            DMemory[6] = 8'h99;
            DMemory[7] = 8'h55;
        end
    end
end
endmodule

module Sign_Extension (sign_in, sign_out);
    input [4:0] sign_in;
    output [7:0] sign_out;
    assign sign_out[4:0]=sign_in[4:0];
    assign sign_out[7:5]=sign_in[4]?{3{1'b1}}:3'b0;
endmodule

```


III.5 EXPERIMENT NO. 5

III.5.1 AIM: To implement I-Type Instruction Beq datapath

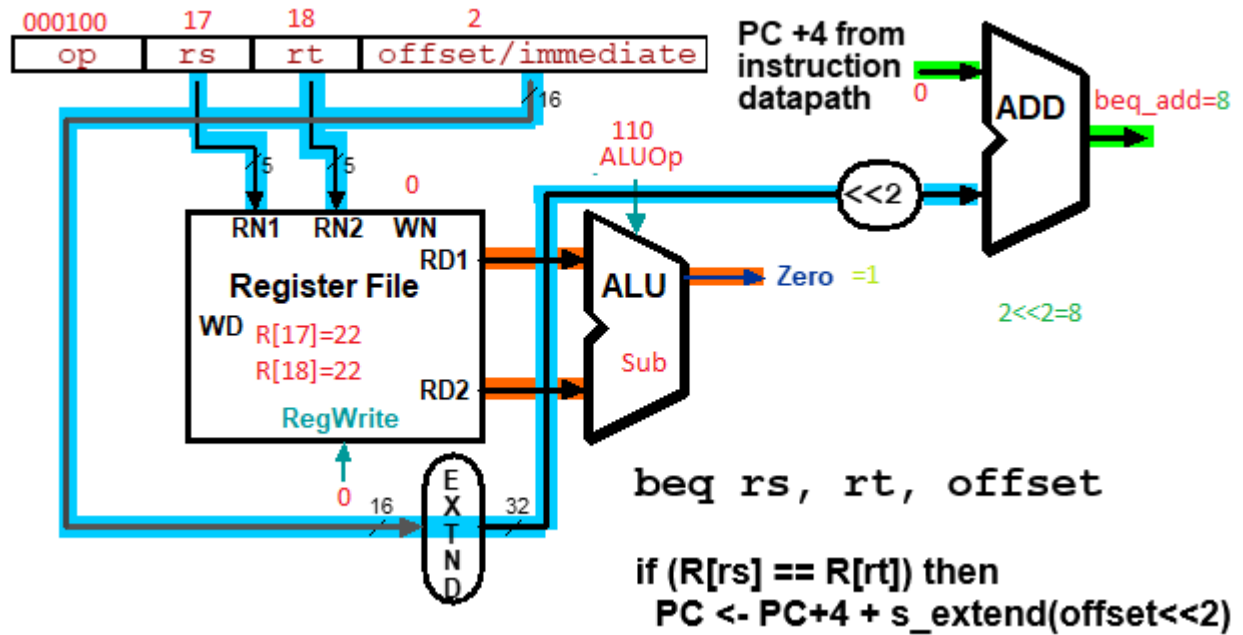

III.5.2 CODE

```
module beq_Datapath (rs,rt,offset,ALUOp,PC_plus_4, Zero,beq_add)
```

```
endmodule
```

III.5.3 LAB ASSIGNMENT

- 1) Write Verilog code to implement beq_Datapath module
- 2) Write testbenches to verify beq_Datapath module, simulate and verify the output data.



III.10.3 LAB ASSIGNMENT

Write testbenches to verify above blocks and attach waveforms.

III. LAB REPORT GUIDELINES

Students write up a report on the Verilog HDL implementation experiment projects created in this lab. The lab report should include Verilog code for the module under test, Verilog test bench code and a truth table results, and example data input and output to validate the experiment. Simulation Result in form of Simulation Capture Screen.