



DIGITAL SYSTEM DESIGN LABORATORY

LAB 7 REPORT

MULTI-CYCLE MICROPROCESSOR DESIGN

NAME: Bùi Gia Bảo
ID: ITITIU22019

I. LAB OBJECTIVES

This Lab experiments are intended to design and test a Multi-Cycle Microprocessor

II. DESCRIPTION

Multi Cycle Microprocessor datapath to be implemented is in figure 2.1.

 


Figure 2.1: Multi-cyclye Cycle Microprocessor DataPath


III. LAB PROCEDURE

III.1 EXPERIMENT NO. 1

III.1.1 AIM: To understand and write the assembly codes using MIPS Instruction Instruction Operation codes:

Op	Opcode name	Value
000000	R-format	R-Type
000010	jmp	J-Type
000100	beq	I-Type
100011	lw	
101011	sw	
010000	addi	

Instruction Formats:

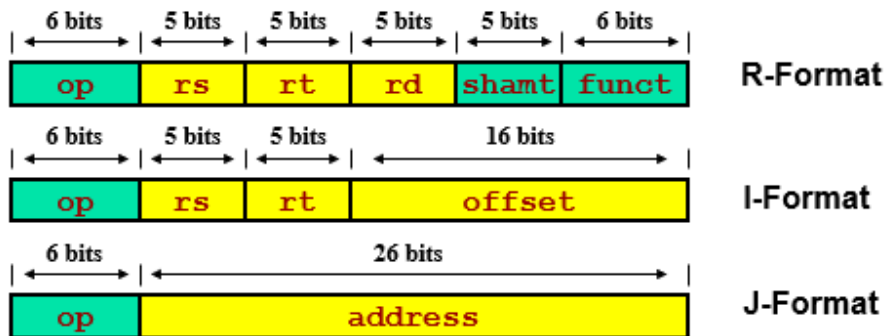

Name	Format	Example						Comments
add	R	0	18	19	17	0	32	add \$s1,\$s2,\$s3
sub	R	0	18	19	17	0	34	sub \$s1,\$s2,\$s3
addi	I	8	18	17	100			addi \$s1,\$s2,100
lw	I	35	18	17	100			lw \$s1,100(\$s2)
sw	I	43	18	17	100			sw \$s1,100(\$s2)
Field size		6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	All MIPS instructions are 32 bits long
R-format	R	op	rs	rt	rd	shamt	funct	Arithmetic instruction format
I-format	I	op	rs	rt	address			Data transfer format

Register names and orders:

Name	Register number	Usage
\$zero	0	the constant value 0
\$v0-\$v1	2-3	values for results and expression evaluation
\$a0-\$a3	4-7	arguments
\$t0-\$t7	8-15	temporaries
\$s0-\$s7	16-23	saved (by callee)
\$t8-\$t9	24-25	more temporaries
\$gp	28	global pointer
\$sp	29	stack pointer
\$fp	30	frame pointer
\$ra	31	return address

Assume the Assembly code code start from address PC=0x00000000, one instruction is store in one memory location.

Testing Assembly Program 1:

	<u>Instruction</u>	<u>Meaning</u>
Begin:	addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2
	addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3
	addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5
	add \$s4, \$s2, \$s3 //	$\$s4 = \$s2 + \$s3 \Rightarrow R20=0x77$
	sub \$s1, \$s2, \$s3 //	$\$s1 = \$s2 - \$s3 \Rightarrow R17=0x22$
	sw \$s1, 0x02(\$s2) //	Memory[\$s2+0x02] = \$s1
	lw \$s6, 0x02(\$s2) //	$\$s6 = \text{Memory}[\$s2+0x02]$
	bne \$s5, \$s4, End //	Next instr. is at End if \$s5 != \$s4
	addi \$s8, \$zero, 0x10 //	load immediate value 10 to register \$s8
	beq \$s5,\$s4, End //	Next instr. is at End if \$s7 == \$s4
	addi \$s8, \$zero, 0x20 //	load immediate value 20 to register \$s8
End:	j End //	jump End

Testing Assembly Program 2:


	<u>Instruction</u>	<u>Meaning</u>
Begin:	addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2
	addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3
	addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5
	add \$s4, \$s2, \$s3 //	$\$s4 = \$s2 + \$s3 \Rightarrow R20=0x77$
	sub \$s1, \$s2, \$s3 //	$\$s1 = \$s2 - \$s3 \Rightarrow R17=0x22$
	sw \$s1, 0x02(\$s2) //	Memory[\$s2+0x02] = \$s1
	lw \$s6, 0x02(\$s2) //	$\$s6 = \text{Memory}[\$s2+0x02]$
	beq \$s5,\$s4, End //	Next instr. is at End if \$s7 == \$s4
	addi \$s8, \$zero, 0x10 //	load immediate value 10 to register \$s8
	bne \$s5, \$s4, End //	Next instr. is at End if \$s5 != \$s4
	addi \$s8, \$zero, 0x20 //	load immediate value 20 to register \$s8
End:	j End //	jump End

III.1.2 LAB ASSIGNMENT

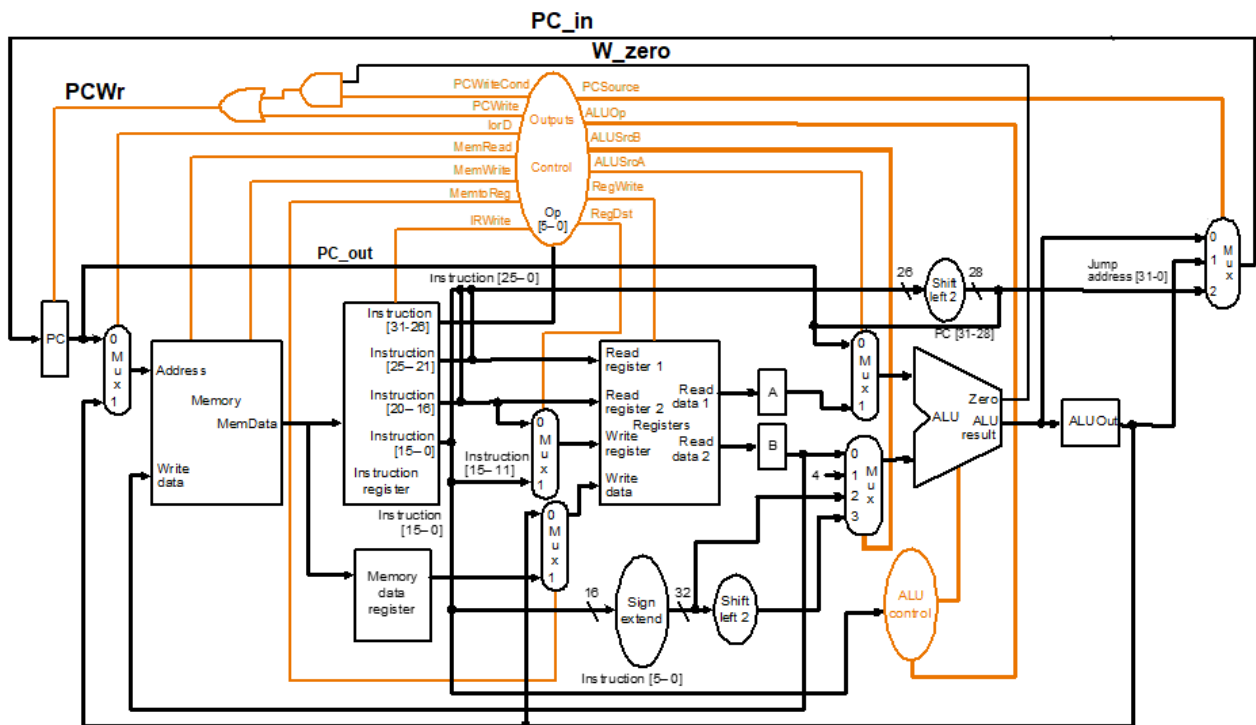- 1) Compile the Assembly **Testing Assembly Program 1** into machine code (decimal code and binary code)
- 2) What is the value of Register \$s8 after running **Testing Assembly Program 1** program
- 3) Compile the Assembly **Testing Assembly Program 2** into machine code (decimal code and binary code)
- 4) What is the value of Register \$s8 after running **Testing Assembly Program 2** program

III.2 EXPERIMENT NO. 2

III.2.1 AIM: To implement Verilog code to test ALL the Components of Multi-Cycle processor



III.4 EXPERIMENT NO. 4

III.4.1 AIM: To Write Verilog code to implement the complete Multi-Cycle processor.

Op	Opcode name	Value
000000	R-format	R-Type
000010	jmp	J-Type
000100	beq	I-Type
100011	lw	
101011	sw	
010000	addi	

III.4.2 CODE

```
module lab7(SW,LEDG,LEDR,  
HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7);  
    input  [17:0] SW;  
    output[17:0] LEDR;  
    output[7:0] LEDG;
```

```
output [0:6] HEX0,HEX1,HEX2,HEX3,HEX4,HEX5,HEX6,HEX7;  
wire [31:0] w_hex;
```

```
Datapath_Multi_cycle_Processor dut(.clk(SW[17]),  
.in_reset(SW[16]),.instruction(w_hex), .state(LED[3:0]));
```

```
HEX_7SEG_DECODE H0(.BIN(w_hex[3:0]), .SSD(HEX0));  
HEX_7SEG_DECODE H1(.BIN(w_hex[7:4]), .SSD(HEX1));  
HEX_7SEG_DECODE H2(.BIN(w_hex[11:8]), .SSD(HEX2));  
HEX_7SEG_DECODE H3(.BIN(w_hex[15:12]), .SSD(HEX3));  
HEX_7SEG_DECODE H4(.BIN(w_hex[19:16]), .SSD(HEX4));  
HEX_7SEG_DECODE H5(.BIN(w_hex[23:20]), .SSD(HEX5));  
HEX_7SEG_DECODE H6(.BIN(w_hex[27:24]), .SSD(HEX6));  
HEX_7SEG_DECODE H7(.BIN(w_hex[31:28]), .SSD(HEX7));
```

```
endmodule
```

```
module HEX_7SEG_DECODE(BIN, SSD);
```

```
input [3:0] BIN;
```

```
output reg [0:6] SSD;
```

```
always begin
```

```
case(BIN)
```

```
0:SSD=7'b0000001;
```

```
1:SSD=7'b1001111;
```

```
2:SSD=7'b0010010;
```

```
3:SSD=7'b0000110;
```

```
4:SSD=7'b1001100;
```

```
5:SSD=7'b0100100;
```

```
6:SSD=7'b0100000;
```

```
7:SSD=7'b0001111;
```

```
8:SSD=7'b0000000;
```

```
9:SSD=7'b0001100;
```

```
10:SSD=7'b0001000;
```

```
11:SSD=7'b1100000;
```

```
12:SSD=7'b0110001;
```

```
13:SSD=7'b1000010;
```

```
14:SSD=7'b0110000;  
15:SSD=7'b0111000;  
endcase  
end  
endmodule  
  
module Datapath_Multi_cycle_Processor(clk, in_reset, instruction, state);  
    input clk;  
    input in_reset;  
    output[3:0] state;  
    wire reset;  
  
    wire[31:0] pc_in;  
    wire[31:0] pc_out;  
  
    wire[31:0] alu_out;  
  
    wire[31:0] addr_in;  
    wire[31:0] Mem_Read_data;  
  
    output[31:0] instruction;  
  
    wire[31:0] MDR_out;  
  
    wire[31:0] ALU_out_hold;  
    wire[31:0] mux_2_out;  
  
    wire[31:0] W_RD1, W_RD2;  
  
    wire[31:0] Extend_out;  
    wire[31:0] Branch_addr;  
    wire[31:0] B_data,A_data;  
    wire[31:0] ALU_in_A;  
    wire[31:0] ALU_in_B;  
    wire[31:0] ALU_out;  
  
    wire [27:0] jump_28_bit;  
  
    wire pc_write;
```

```
wire IorD;  
wire MemRead;  
wire MemWrite;  
wire IRwrite;  
wire MemtoReg;  
wire RegDst;  
wire RegWrite;  
wire ALUSrcA;  
wire ALUSrcB;  
wire zero;  
wire PCWrite;  
wire PCWrcond;
```

```
wire[4:0] mux_3_out;  
wire and_out;
```

```
Program_Counter c1(.clk(clk), .reset(reset), .PC_write(pc_write)  
,.PC_in(pc_in) , .PC_out(pc_out));
```

```
Mux_32_bit c2(.in0(pc_in), .in1(alu_out), .mux_out(addr_in),  
.select(IorD));
```

```
Data_Memory c3(.clk(clk),.addr(addr_in), .write_data(B_data),  
.read_data(Mem_Read_data), .MemRead(MemRead), .MemWrite(MemWrite));
```

```
holding_reg c4(.output_data(instruction), .input_data(Mem_Read_data),  
.write(IRwrite), .clk(clk), .reset(reset));
```

```
holding_reg c5(.output_data(MDR_out), .input_data(Mem_Read_data),  
.write(1'b1), .clk(clk), .reset(reset));
```

```
Mux_32_bit c6(.in0(ALU_out_hold), .in1(MDR_out),  
.mux_out(mux_2_out), .select(MemtoReg));
```

```
Mux_5_bit c7(.in0(instruction[20:16]), .in1(instruction[15:11]),  
.mux_out(mux_3_out), .select(RegDst));
```

```
Register_File c8(      .clk(clk),  
                        .read_addr 1(instruction[25:21]),
```



```

        .read_addr_2(instruction[20:16]),
        .write_addr(mux_3_out),
        .read_data_1(W_RD1),
        .read_data_2(W_RD2),
        .write_data(mux_2_out),
        .RegWrite(RegWrite));

    Sign_Extension c9(.sign_in(instruction[15:0]), .sign_out(Extend_out));

    shift_left_2 c10(.sign_in(Extend_out), .sign_out(Branch_addr));

    holding_reg c11(.output_data(A_data), .input_data(W_RD1), .write(1'b1),
    .clk(clk), .reset(reset));

    holding_reg c12(.output_data(B_data), .input_data(W_RD2), .write(1'b1),
    .clk(clk), .reset(reset));

    Mux_32_bit c13(.in0(pc_out), .in1(A_data), .mux_out(ALU_in_A),
    .select(ALUSrcA));

    Mux4_32_bit c14(.in0(B_data), .in1(32'd4) ,.in2(Extend_out),
    .in3(Branch_addr), .mux_out(ALU_in_B), .select(ALUSrcB));

    alu c15(.alufn(Operation_ALU),
        .ra(ALU_in_A),
        .rb_or_imm(ALU_in_B),
        .aluout(ALU_out),
        .zero(zero));

    ALU_Control c16(.Op_intstruct(instruction[5:0])
    ,.ints_function(Operation_ALU), .ALUOp(ALUop));

    shift_left_2_28bit c17(.sign_in(instruction[25:0]), .sign_out(jump_28_bit));

    holding_reg c18(.output_data(ALU_out_hold), .input_data(ALU_out),
    .write(1'b1), .clk(clk), .reset(reset));

    concatenate
    c19(.PC_in(pc_out[31:28]),.IR_in(jump_28_bit),.PC_out(Jump_addr));

```

```
Mux4_32_bit c20(.in0(ALU_out), .in1(ALU_out_hold) ,.in2(Jump_addr),
.in3(32'b0), .mux_out(pc_in), .select(PCSource));
```

```
controller c21(.in_reset(in_reset)
,.opcode(instruction[31:26])
,.reset(reset)
,.clk(clk)
,.PCWrite(PCWrite)
,.Iord(Iord)
,.MemRead(MemRead)
,.MemWrite(MemWrite)
,.IRwrite(IRwrite)
,.MemtoReg(MemtoReg)
,.RegWrite(RegWrite)
,.RegDst(RegDst)
,.ALUSrcA(ALUSrcA)
,.ALUSrcB(ALUSrcB)
,.PCSource(PCSource)
,.ALUOp(ALUOp)
,.PCWrcond(PCWrcond)
,.state(state));
```

```
and c22(and_out,zero,PCWrcond);
or c23(pc_write,and_out,PCWrite);
```

```
endmodule
```

```
module controller(in_reset,opcode,
reset,clk,PCWrite,Iord,MemRead,MemWrite,IRwrite,MemtoReg,RegWrite,RegD
st,ALUSrcA,ALUSrcB,PCSource,ALUOp,PCWrcond,state);
```

```
// ~~~~~ PORTS ~~~~~ //
```

```
// opcode, clock, and reset inputs
```

```
input [5:0] opcode; // from instruction register
```

```
inputclk,in_reset;
```

```
// control signal outputs
```

```
output reg
```

```
PCWrite,Iord,MemRead,MemWrite,IRwrite,MemtoReg,RegWrite,RegDst,ALUSr
cA;
```

```

output reg [1:0] ALUSrcB,PCSource;
output reg [2:0] ALUOp;
output reg PCWrcond;
output reg reset;
// ~~~~~ REGISTER ~~~~~ //

// 4-bit state register
output reg [3:0] state;

// ~~~~~ PARAMETERS ~~~~~ //

// state parameters
parameter s0 = 4'd0;
parameter s1 = 4'd1;
parameter s2 = 4'd2;
parameter s3 = 4'd3;
parameter s4 = 4'd4;
parameter s5 = 4'd5;
parameter s6 = 4'd6;
parameter s7 = 4'd7;
parameter s8 = 4'd8;
parameter s9 = 4'd9;
parameter s10 = 4'd10;
parameter s_Reset = 4'd11; // reset

// opcode[5:4] parameters
parameter J = 6'b000010; // Jump or NOP
parameter R = 6'b000000; // R-type
parameter BEQ = 6'b000100; // Branch
parameter BNE = 6'b000101; // Branch
parameter SW = 6'b101011; // I-type
parameter LW = 6'b100011; // I-type
parameter ADDI = 6'b001000; // I-type

// OP code control for ALU

parameter OP_R_TYPE = 3'b000;
parameter OP_I_TYPE = 3'b001;

```

```
parameter OP_J_TYPE = 3'b010;
parameter OP_BR_TYPE = 3'b011;
parameter OP_IF_TYPE = 3'b100;
parameter OP_ID_TYPE = 3'b101;
parameter OP_RS_TYPE = 3'b110;

// ~~~~~ STATE MACHINE ~~~~~ //

// control state machine
always @(posedge clk or posedge in_reset)
begin

    // check for reset signal. If set, write zero to PC and switch to Reset State on
    next CC.
    if (in_reset) begin
        PCWrite=0;
        Iord=0;
        MemRead=1;
        MemWrite=0;
        IRwrite=1;
        MemtoReg=0;
        RegWrite=0;
        RegDst=0;
        ALUSrcA=0;
        ALUSrcB=2'b01;
        PCSrc=2'b00;
        ALUOp=OP_RS_TYPE;
        PCWrcond=0;
        reset =1;
        state <= s_Reset;
    end
    else
    begin // if reset signal is not set, check state at pos edge
        case (state)
            s_Reset:
                begin
                    PCWrite=0;
                    Iord=0;
                    MemRead=1;
                    MemWrite=0;
```

```
IRwrite=1;
MemtoReg=0;
RegWrite=0;
RegDst=0;
ALUSrcA=0;
ALUSrcB=2'b01;
PCSource=2'b00;
ALUOp=OP_RS_TYPE;
PCWrcond=0;
reset =0;
state <= s0;
$display("state Reset");
end
s0:
begin
Iord=0;
MemRead=1;
MemWrite=0;
IRwrite=1;
MemtoReg=0;
RegWrite=0;
RegDst=0;
ALUSrcA=0;
ALUSrcB=2'b01;
PCSource=2'b00;
ALUOp=OP_IF_TYPE;
PCWrcond=0;
state <= s1;
PCWrite=1;
$display("state 0");
end
s1:
begin
PCWrite=0;
Iord=0;
MemRead=0;
MemWrite=0;
IRwrite=0;
MemtoReg=0;
RegWrite=0;
RegDst=0;
```

```
ALUSrcA=0;
ALUSrcB=2'b11;
PCSource=2'b00;
ALUOp=OP_ID_TYPE;
PCWrcond=0;
$display("state 1");
case(opcode[5:0])
  J: state <= s9;
  R: state <= s6;
  SW: state <= s2;
      LW: state <= s2;
      ADDI: state <= s2;
  BEQ: state <= s8;
endcase
end
```

```
s2:
begin
  PCWrite=0;
  Iord=1;
  MemRead=1;
  MemWrite=0;
  IRwrite=0;
  MemtoReg=0;
  RegWrite=0;
  RegDst=0;
  ALUSrcA=1;
  ALUSrcB=2'b10;
  PCSource=2'b00;
  ALUOp=OP_I_TYPE;
  PCWrcond=0;
  $display("state 2");
  if(opcode[5:0]== ADDI)
    begin
      state <= s10;
      $display("ADDI state");
    end
  else if(opcode[5:0]== SW)
    begin
      state <= s5;
      $display("SW state");
```

```
        end
    else
        begin
            state <= s3;
            $display("SW state");
        end
    $display("state 2");
end
s3:
begin
    PCWrite=0;
    Iord=1;
    MemRead=1;
    MemWrite=0;
    IRwrite=0;
    MemtoReg=0;
    RegWrite=0;
    RegDst=0;
    ALUSrcA=1;
    ALUSrcB=2'b10;
    PCSource=2'b00;
    ALUOp=OP_I_TYPE;
    PCWrcond=0;
    state <= s4;
    $display("state 3");
end
s4:
begin
    PCWrite=0;
    Iord=1;
    MemRead=0;
    MemWrite=0;
    IRwrite=0;
    MemtoReg=0;
    RegWrite=1;
    RegDst=0;
    ALUSrcA=0;
    ALUSrcB=2'b10;
    PCSource=2'b00;
    ALUOp=OP_I_TYPE;
    PCWrcond=0;
```

```
state <= s0;
$display("state 4");
end
s5:
begin
PCWrite=0;
Iord=1;
MemRead=0;
MemWrite=1;
IRwrite=0;
MemtoReg=0;
RegWrite=0;
RegDst=0;
ALUSrcA=0;
ALUSrcB=2'b10;
PCSource=2'b00;
ALUOp=OP_I_TYPE;
PCWrcond=0;
state <= s0;
$display("state 5");
end

s6:
begin
PCWrite=0;
Iord=0;
MemRead=0;
MemWrite=0;
IRwrite=0;
MemtoReg=0;
RegWrite=0;
RegDst=0;
ALUSrcA=1;
ALUSrcB=2'b00;
PCSource=2'b00;
ALUOp=OP_R_TYPE;
PCWrcond=0;
state <= s7;
$display("state 6");
end
```



```
s7:
begin
  PCWrite=0;
  Iord=0;
  MemRead=0;
  MemWrite=0;
  IRwrite=0;
  MemtoReg=1;
  RegWrite=1;
  RegDst=1;
  ALUSrcA=1;
  ALUSrcB=2'b00;
  PCSource=2'b00;
  ALUOp=OP_R_TYPE;
  PCWrcond=0;
  state <= s0;
  $display("state 7");
end

s8:
begin
  PCWrite=0;
  Iord=0;
  MemRead=0;
  MemWrite=0;
  IRwrite=0;
  MemtoReg=0;
  RegWrite=0;
  RegDst=0;
  ALUSrcA=1;
  ALUSrcB=2'b00;
  PCSource=2'b01;
  ALUOp=OP_BR_TYPE;
  PCWrcond=1;
  state <= s0;
  $display("state 8");
end

s9:
begin
  PCWrite=1;
```

```
Iord=0;
MemRead=0;
MemWrite=0;
IRwrite=0;
MemtoReg=0;
RegWrite=0;
RegDst=0;
ALUSrcA=1;
ALUSrcB=2'b00;
PCSource=2'b10;
ALUOp=OP_J_TYPE;
PCWrcond=0;
state <= s0;
$display("state 9");
end
s10:
begin
  PCWrite=0;
  Iord=0;
  MemRead=0;
  MemWrite=0;
  IRwrite=0;
  MemtoReg=1;
  RegWrite=1;
  RegDst=0;
  ALUSrcA=1;
  ALUSrcB=2'b00;
  PCSource=2'b00;
  ALUOp=OP_R_TYPE;
  PCWrcond=0;
  state <= s0;
  $display("state 7");
end
default: begin
  PCWrite=0;
  Iord=0;
  MemRead=0;
  MemWrite=0;
  IRwrite=0;
  MemtoReg=0;
  RegWrite=0;
```

```
RegDst=0;
ALUSrcA=0;
ALUSrcB=2'b01;
PCSource=2'b00;
ALUOp=OP_RS_TYPE;
PCWrcond=0;
$display("state default control");
state <= s_Reset;
end
endcase
end
end
endmodule

module ALU_Control(Op_intstruct,ints_function,ALUOp);
    input [5:0] ints_function;
    input [2:0] Op_intstruct;
    output reg [2:0] ALUOp;
    // OP code control for ALU

    parameter OP_R_TYPE = 3'b000;
    parameter OP_I_TYPE = 3'b001;
    parameter OP_J_TYPE = 3'b010;
    parameter OP_BR_TYPE = 3'b011;
    parameter OP_IF_TYPE = 3'b100;
    parameter OP_ID_TYPE = 3'b101;
    parameter OP_RS_TYPE = 3'b110;

    always @(*)
    begin
        case(Op_intstruct)
            OP_R_TYPE: // R-Type Instruction look at fuction
            begin
                ALUOp = 3'b000;
                if(ints_function==6'b100000) // add
                begin
                    ALUOp = 3'b000;
                    $display("fuction Add");
                end

                if(ints_function==6'b100010) // sub
```

```
begin
    ALUOp =3'b001;
    $display("fuction sub");
end

if(ints_function==6'b100100) // and
begin
    ALUOp =3'b010;
    $display("fuction and");
end

if(ints_function==6'b100101) // or
begin
    ALUOp =3'b010;
    $display("fuction or ");
end
end
OP_I_TYPE:
begin
    ALUOp =3'b000;
    $display("LW or SW");
end
OP_J_TYPE:
begin
    ALUOp =3'b000;
    $display("Jump");
end
OP_BR_TYPE: // beq instruction
begin
    ALUOp =3'b111;
    $display("BEQ or BNE");
end
OP_IF_TYPE: // Store Instruction
begin
    ALUOp =3'b000;
    $display("Add IF");
end
OP_ID_TYPE: // addi Instruction
begin
    ALUOp =3'b000;
    $display("add ID");
```

```
end
OP_RS_TYPE: //bne
begin
    ALUOp =3'b111;
    $display("Reset OP");
end
default :
begin
    ALUOp =3'b000;
    $display("ALU default");
end
endcase
end
endmodule

module Mux_5_bit (in0, in1, mux_out, select);
    parameter N = 5;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select? in1: in0 ;
endmodule

module Sign_Extension (sign_in, sign_out);
    input [15:0] sign_in;
    output [31:0] sign_out;
    assign sign_out[15:0]=sign_in[15:0];
    assign sign_out[31:16]=sign_in[15]?16'b1111_1111_1111_1111:16'b0;
endmodule

module Program_Counter (clk, reset,PC_write ,PC_in, PC_out);
    input clk, reset,PC_write;
    input [31:0] PC_in;
    output reg [31:0] PC_out;
    always @ (posedge clk or posedge reset)
    begin
        if(reset==1'b1)
            PC_out<=0;
        else if (PC_write==1'b1)
            PC_out<=PC_in;
    end
endmodule
```

```

module alu(
    input [2:0] alufn,
    input [31:0] ra,
    input [31:0] rb_or_imm,
    output reg [31:0] aluout,
    output reg zero);
    parameter  ALU_OP_ADD      = 3'b000,
               ALU_OP_SUB      = 3'b001,
               ALU_OP_AND      = 3'b010,
               ALU_OP_OR       = 3'b011,
               ALU_OP_XOR      = 3'b100,
               ALU_OP_LW       = 3'b101,
               ALU_OP_SW       = 3'b110,
               ALU_OP_BEQ      = 3'b111;

    always @(*)
        begin
            case(alufn)
                ALU_OP_ADD      : aluout = ra + rb_or_imm;
                ALU_OP_SUB      : aluout = ra - rb_or_imm;
                ALU_OP_AND      : aluout = ra & rb_or_imm;
                ALU_OP_OR       : aluout = ra | rb_or_imm;
                ALU_OP_XOR      : aluout = ra ^ rb_or_imm;
                ALU_OP_LW       : aluout = ra + rb_or_imm;
                ALU_OP_SW       : aluout = ra + rb_or_imm;
                ALU_OP_BEQ      : begin
                                zero = (ra==rb_or_imm)?1'b1:1'b0;
                                aluout = ra - rb_or_imm;
                                end
            endcase
        end
    end
endmodule

module Register_File (clk,read_addr_1, read_addr_2, write_addr, read_data_1,
read_data_2, write_data, RegWrite);
    input [4:0] read_addr_1, read_addr_2, write_addr;
    input [31:0] write_data;
    input clk,RegWrite;
    reg checkRegWrite;
    output reg [31:0] read_data_1, read_data_2;

```

```
reg [31:0] Regfile [31:0];
integer k;
initial
begin
    for (k=0; k<32; k=k+1)
        begin
            Regfile[k] = 32'd10;
        end
    Regfile[8]=32'd1;
    Regfile[9]=32'd2;
    Regfile[10]=32'd3; //$t2
    Regfile[11]=32'd4; //$t3

    Regfile[17]=32'd99;
    Regfile[18]=32'd60;
    Regfile[19]=32'd30;
end

//assign read_data_1 = Regfile[read_addr_1];
always @(read_data_1 or Regfile[read_addr_1])
begin
    if (read_addr_1 == 0) read_data_1 = 0;
    else
        begin
            read_data_1 = Regfile[read_addr_1];
        end
end

//$display("read_addr_1=%d,read_data_1=%h",read_addr_1,read_data_1);

//assign read_data_2 = Regfile[read_addr_2];
always @(read_data_2 or Regfile[read_addr_2])
begin
    if (read_addr_2 == 0) read_data_2 = 0;
    else
        begin
            read_data_2 = Regfile[read_addr_2];
        end
end

//$display("read_addr_2=%d,read_data_2=%h",read_addr_2,read_data_2);

end
```

```
always @(posedge clk)
begin
    if (RegWrite == 1'b1)
        begin
            Regfile[write_addr] = write_data;
            $display("Rigister File write_addr=%d
write_data=%d",write_addr,write_data);
        end
    end
endmodule

module holding_reg (
    output reg [31:0] output_data,
    input    [31:0] input_data,
    input    write,
    input    clk,
    input    reset
);

always @(posedge clk or posedge reset) begin
    if (reset)
        output_data <= 32'b0;
    else if (write)
        output_data <= input_data;
end

endmodule

module Mux_32_bit (in0, in1, mux_out, select);
    parameter N = 32;
    input [N-1:0] in0, in1;
    output [N-1:0] mux_out;
    input select;
    assign mux_out = select? in1: in0 ;
endmodule

module shift_left_2 (sign_in, sign_out);
    input [31:0] sign_in;
    output [31:0] sign_out;
    assign sign_out[31:2]=sign_in[29:0];
    assign sign_out[1:0]=2'b00;
```



```
endmodule
```

```
module concat(PC_in,IR_in,PC_out);  
    input [3:0] PC_in;  
    input [27:0] IR_in;  
    output[31:0] PC_out;  
    assign PC_out={PC_in, IR_in};  
endmodule
```

```
module Mux4_32_bit (in0, in1,in2, in3, mux_out, select);  
    parameter N = 32;  
    input [N-1:0] in0, in1,in2,in3;  
    output [N-1:0] mux_out;  
    input [1:0]select;  
    assign mux_out = select[1]? (select[0]?in3: in2):(select[0]?in1:in0);  
endmodule
```

```
module shift_left_2_28bit (sign_in, sign_out);  
    input [25:0] sign_in;  
    output [27:0] sign_out;  
    assign sign_out={2'b00,sign_in};  
endmodule
```

```
module Data_Memory (clk,addr, write_data, read_data, MemRead, MemWrite);  
    input [31:0] addr;  
    input [31:0] write_data;  
    output [31:0] read_data;  
    input MemRead, MemWrite,clk;  
    reg [31:0] DMemory [63:0];  
    integer k;  
    initial begin  
        for (k=0; k<64; k=k+1)  
            begin  
                DMemory[k] = 32'b0;  
            end  
        //sw $s1, 0x02($s2)    // Memory[$s2+0x02] = $s1  
        DMemory[0] = 32'b10101110010100010000000000000010;  
  
        //add $s4, $s2, $s3    // $s4 = $s2 + $s3 => R20=0x90  
        DMemory[4] = 32'b000000010010100111010000000100000;
```

```

//add $s5 $t0 $t1
DMemory[8] = 32'b000000001000010011010100000100000;

//sub $s1, $s2, $s3    // $s1 = $s2 - $s3 => R17=0x22
DMemory[12] = 32'b000000010010100111000100000100010;

//sw $s1, 0x02($s2)    // Memory[$s2+0x02] = $s1
DMemory[16] = 32'b101011100101000100000000000000010;

//lw $s1, 0x02($s2)    // $s1 = Memory[$s2+0x02]
DMemory[20] = 32'b100011100101000100000000000000010;

//beq $t2,$t3, End    //beq $t2,$t3, 0x03
DMemory[24] = 32'b000100010100101100000000000000011;

//addi $s7, $zero, 0x10
DMemory[28] = 32'b0010000000001011100000000000010000;
    //j 0x00
DMemory[32] = 32'b000010000000000000000000000000000;
//addi $s2, $zero, 0x55 // load immediate value 0x55 to register $s2
DMemory[36] = 32'b0010000000001001000000000001010101;
//addi $s3, $zero, 0x22 // load immediate value 0x22 to register $s3
DMemory[40] = 32'b0010000000001001100000000000100010;
//addi $s5, $zero, 0x77 // load immediate value 0x77 to register $s5
DMemory[44] = 32'b0010000000001010100000000001110111;
end

assign read_data = (MemRead) ? DMemory[addr] : 32'bx;


always @(posedge clk)
begin
    if (MemWrite)
    begin
        DMemory[addr] = write_data;
        $display("Data memory write_addr=%d",
write_data=%d",addr,write_data);
    end
end

```

end
endmodule

III.4.3 LAB ASSIGNMENT

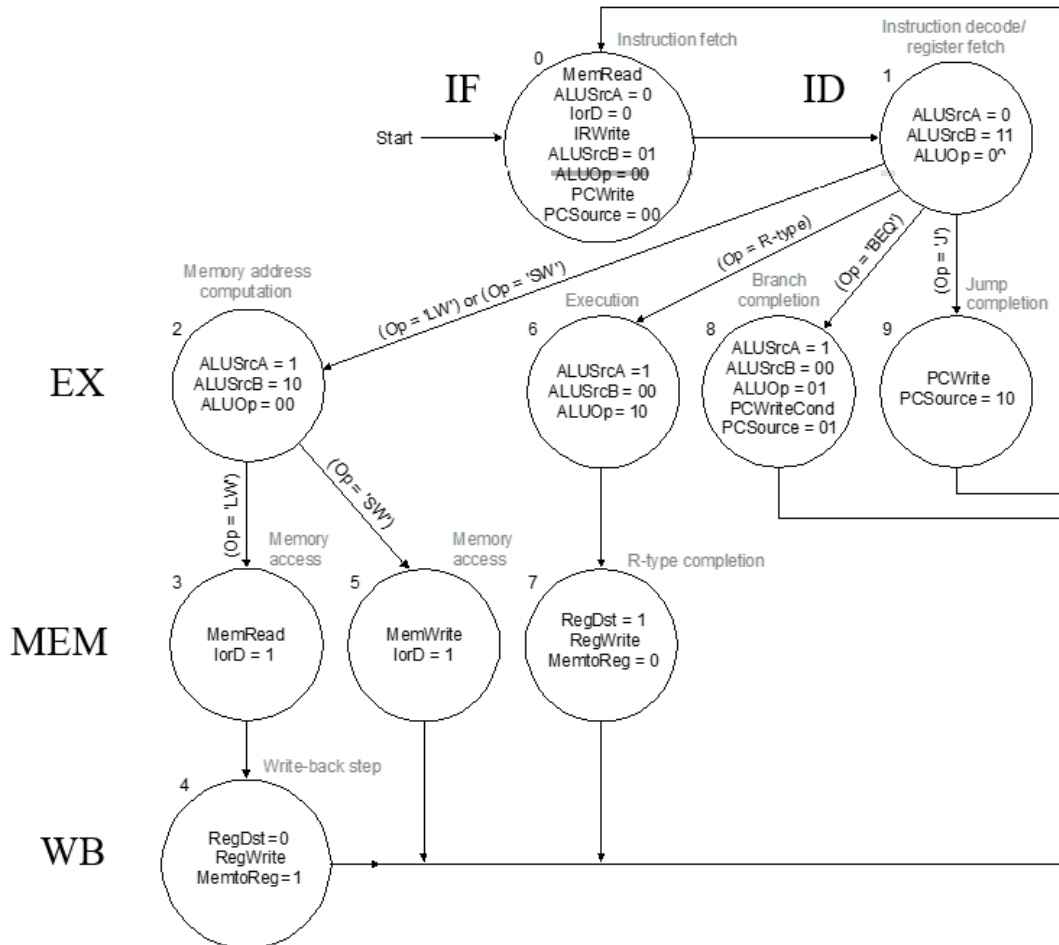1) Write the Verilog code to implement the Microprocessor Control module using FSM with the following State graph:




2) Write the ALU control module with the following input and output truth table:

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

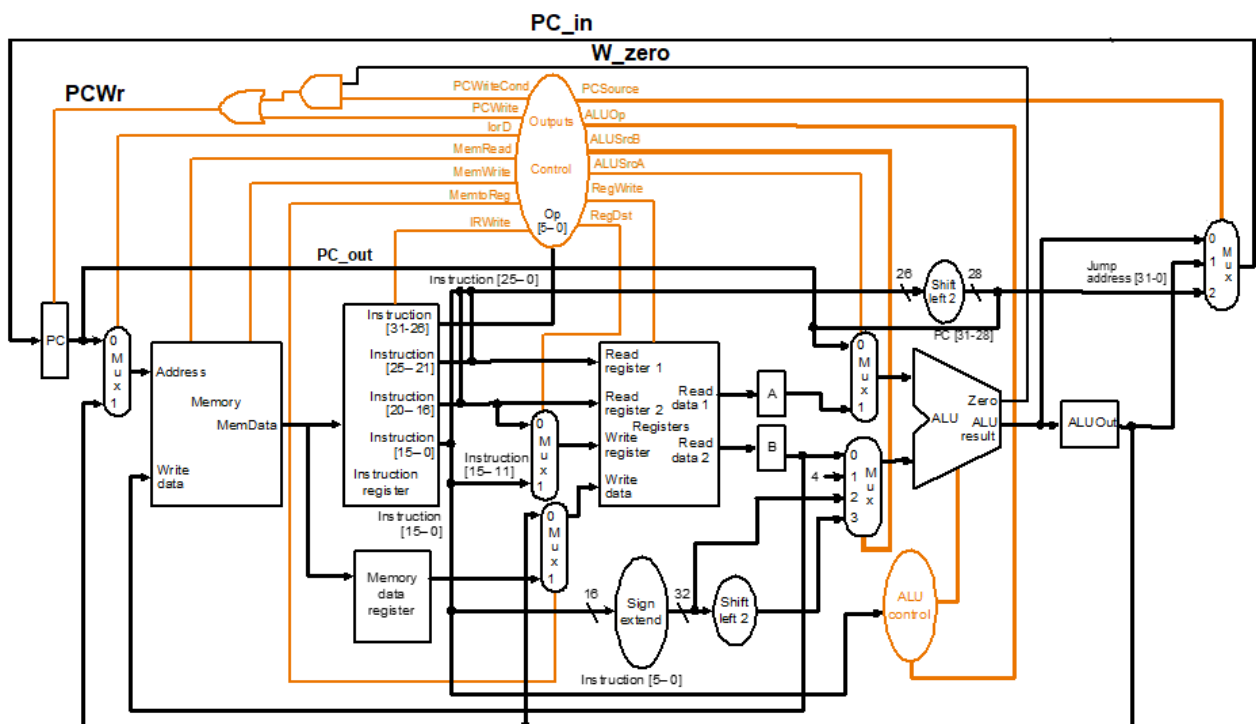3) Write Verilog code to implement complete Multi-Cycle Processor module



4) Write following Assembly code and compile into binary machine code to verify Instruction execution and Datapath operation of the complete Multi-Cycle Processor, write the testbench simulate and check the simulation output data.

```
add $s4, $s2, $s3    // $s4 = $s2 + $s3
sub $s1, $s2, $s3    // $s1 = $s2 - $s3
and $s4, $s2, $s3    // $s4 = $s2 + $s3
or  $s1, $s2, $s3    // $s1 = $s2 - $s3
```

5) Write following Assembly code and compile into binary machine code to verify SW and LW Instruction execution and Datapath operation of the complete Multi-Cycle Processor, write the testbench simulate and check the simulation output data.

```
sw $s1, 0x02($s2)    // Memory[$s2+0x02] = $s1
lw $s6, 0x02($s2)    // $s6 = Memory[$s2+0x02]
```

6) Write following Assembly code and compile into binary machine code to verify beq and bne Instruction execution and Datapath operation of the complete Multi-Cycle Processor, write the testbench simulate and check the simulation output data.

```
bne $s5, $s4, End    // Next instr. is at End if $s5 != $s4
add $s4, $s2, $s3//
beq $s5,$s4, End      // Next instr. is at End if $s7 == $s4
add $s4, $s2, $s3
```

End:

7) Compile the following code into binary machine code and store in Instruction memory to test the complete Multi-Cycle Complete Processor.

Testing Assembly Program 1:

	<u>Instruction</u>	<u>Meaning</u>
Begin:	addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2 R18
	addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3 R19
	addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5 R21
	add \$s4, \$s2, \$s3 //	\$s4 = \$s2 + \$s3 => R20=R18+R19 = 0x77
	sub \$s1, \$s2, \$s3 //	\$s1 = \$s2 - \$s3 => R17=R18-R19=0x33
	sw \$s1, 0x02(\$s2) //	Memory[0x55+0x02] = \$s1 0x33 => RAM[0x57]
	lw \$s6, 0x02(\$s2) //	\$s6 = Memory[\$s2+0x02]
	bne \$s5, \$s4, End //	Next instr. is at End if \$s5 != \$s4
	addi \$s8, \$zero, 0x10 //	load immediate value 10 to register \$s8
	beq \$s5,\$s4, End //	Next instr. is at End if \$s7 == \$s4
	addi \$s8, \$zero, 0x20 //	load immediate value 20 to register \$s8
End:	j End //	jump End

8) Compile the following code into binary machine code and store in Instruction memory to test the Complete Multi-Cycle Processor.

Testing Assembly Program 2:

	<u>Instruction</u>	<u>Meaning</u>
Begin:	addi \$s2, \$zero, 0x55 //	load immediate value 0x55 to register \$s2
	addi \$s3, \$zero, 0x22 //	load immediate value 0x22 to register \$s3
	addi \$s5, \$zero, 0x77 //	load immediate value 0x77 to register \$s5



```
add $s4, $s2, $s3    // $s4 = $s2 + $s3 => R20=0x77
sub $s1, $s2, $s3    // $s1 = $s2 - $s3 => R17=0x22
sw $s1, 0x02($s2)    // Memory[$s2+0x02] = $s1
lw $s6, 0x02($s2)    // $s6 = Memory[$s2+0x02]
beq $s5,$s4, End    // Next instr. is at End if $s7 == $s4
addi $s8, $zero, 0x10 // load immediate value 10 to register $s8
bne $s5, $s4, End    // Next instr. is at End if $s5 != $s4
addi $s8, $zero, 0x20 // load immediate value 20 to register $s8
End: j End           // jump End
```

9) Write the assembly code to carry following calculation formula
Sum = 1+2+3+9;

Compile the following code into binary machine code and store in Instruction memory to test the Complete Multi-cycle Processor.

III. LAB REPORT GUIDELINES

Students write up a report on the Verilog HDL implementation experiment projects created in this lab. The lab report should include Assembly Testing code, Verilog code for the module under test, Verilog test bench code and a truth table results, and example data input and output to validate the experiment. Simulation Result in form of Simulation Capture Screen. Analyzing the Calculation.